



Inspiring Excellence

Experiment number: 04

Name of the experiment : Application of k-Map Method

Group number : 03

Group members names and ids:

1. Md.Abu Hanif Siam . (21301755)
2. Vaskor Debnath. (21301211)
3. Mahmud Ferdous. (21301401)
4. Md.Tasnim Muttaki. (21101216)

Name of the Experiment: Application of K-Map method.



Objective:

- To investigate the rules of K-map
- To gain experience working with practical circuits.
- To simplify a complex function using K-map.

Required Components and Equipments

- AT-200 Portable Analog/Digital Laboratory
- AND, OR, NOT, XOR IC

Experimental Setup:

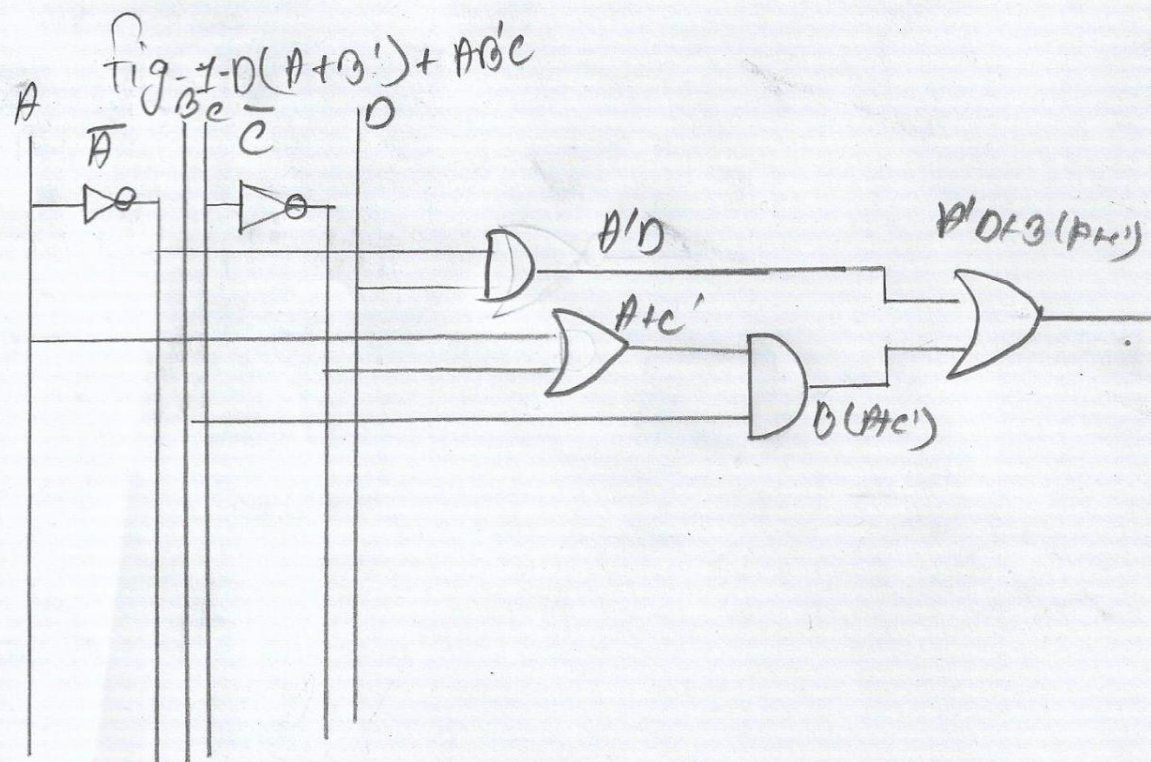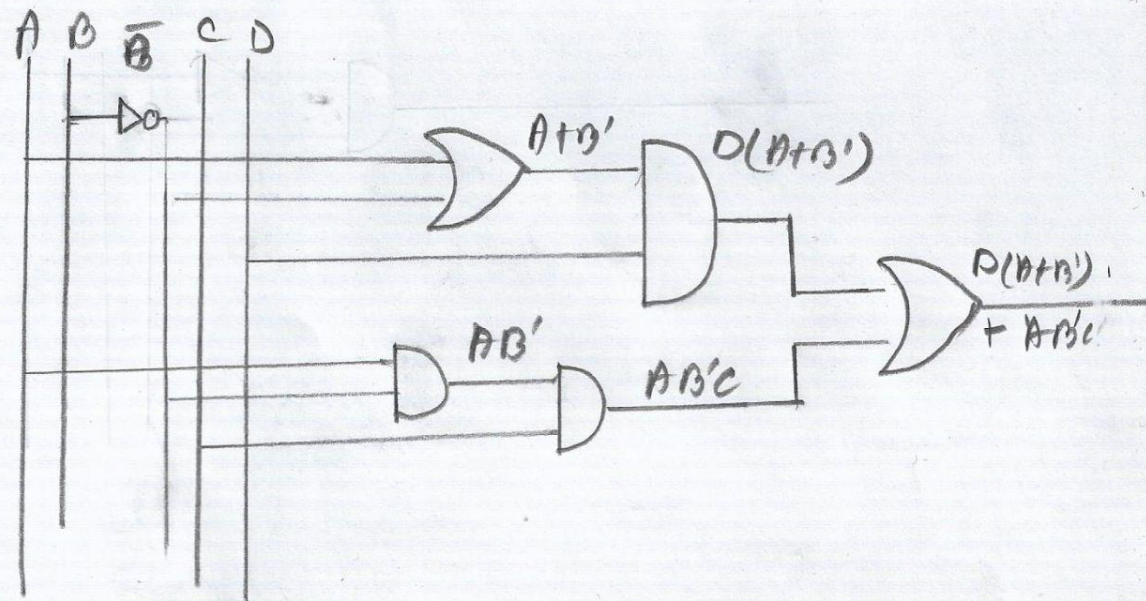

#Results:

Given function - $f =$

$$f(A, B, C, D) = \sum(1, 3, 9, 10, 11, 13, 15)$$

$$= \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{C}D + A\bar{B}C\bar{D} + A\bar{B}C\bar{D} + A\bar{B}\bar{C}D + A\bar{B}C\bar{D}$$

	$\begin{smallmatrix} \bar{C}D \\ 00 \end{smallmatrix}$	$\begin{smallmatrix} C'D \\ 01 \end{smallmatrix}$	$\begin{smallmatrix} CD \\ 11 \end{smallmatrix}$	$\begin{smallmatrix} C\bar{D} \\ 10 \end{smallmatrix}$
$\begin{smallmatrix} \bar{A}B \\ 00 \end{smallmatrix}$		1	3	2
$\begin{smallmatrix} \bar{A}B \\ 01 \end{smallmatrix}$	4	5	7	6
$\begin{smallmatrix} AB \\ 11 \end{smallmatrix}$	12	13	15	14
$\begin{smallmatrix} AB \\ 10 \end{smallmatrix}$	8	9	11	10

$$\therefore F = AD + B'D + AB'C$$

$$= D(A+B') + AB'C$$

Truth Table 1

A	B	C	D	\bar{A}	\bar{B}	\bar{C}	\bar{D}	$D(A+B)^D$	$A \cdot B \cdot C$	$A(A+B) + A \cdot B \cdot C$
0	0	0	0	1	1	1	1	0	0	0
0	0	0	1	1	1	1	0	1	0	1
0	0	1	0	1	1	0	1	0	0	0
0	0	1	1	1	1	0	0	1	0	1
0	1	0	0	1	0	1	1	0	0	0
0	1	0	1	1	0	1	0	0	0	0
0	1	1	0	1	0	0	1	0	0	0
0	1	1	1	1	0	0	0	0	0	0
1	0	0	0	0	1	1	1	0	0	0
1	0	0	1	0	1	1	0	1	0	1
1	0	1	0	0	1	0	1	0	0	0
1	0	1	1	0	1	0	0	1	0	1
1	1	0	0	0	0	1	1	0	0	0
1	1	0	1	0	0	1	0	1	0	1
1	1	1	0	0	0	0	1	0	0	0
1	1	1	1	0	0	0	0	1	0	1

Given function - 2

$$F(A, B, C, D) = \sum (1, 4, 5) + d(3, 5, 7, 12, 13, 14)$$

$$F(A, B, C, D) = \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}\bar{D} + AB\bar{C}D$$

$$d(A, B, C, D) = (3, 5, 7, 12, 13, 14)$$

$$= \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} + AB\bar{C}\bar{D} + AB\bar{C}D + AB\bar{C}\bar{D}$$

	$\frac{00}{CD}$	$\frac{01}{CD}$	$\frac{11}{CD}$	$\frac{10}{CD}$
$\frac{00}{AB}$	0	1	X / 3	2
$\frac{01}{AB}$	1	X	X / 7	6
$\frac{10}{AB}$	X	X	1	X
$\frac{11}{AB}$				

$$\therefore F = A'D + B\bar{C} + AB$$

$$= A'D + B(\bar{C} + A)$$

Truth Table - 2

on	A	B	C	D	\overline{A}	\overline{B}	\overline{C}	\overline{D}	$A\overline{B}$	$B(\overline{C}+A)$	$A\overline{B}+B(\overline{C}+A)$
1	0	0	0	0	1	1	1	1	0	0	0
2	0	0	0	1	1	1	1	0	1	0	1
3	0	0	1	0	1	1	0	1	0	0	0
4	0	0	1	1	1	1	0	0	1	0	1
5	0	1	0	0	1	0	1	1	0	1	1
6	0	1	0	1	1	0	1	0	1	1	1
7	0	1	1	0	1	0	0	1	0	0	0
8	0	1	1	1	1	0	0	0	1	0	1
9	1	0	0	0	0	1	1	1	0	1	1
10	1	0	0	1	0	1	1	0	0	1	1
11	1	0	1	0	0	1	0	1	0	1	1
12	1	0	1	1	0	1	0	0	0	1	1
13	1	1	0	0	0	0	1	1	0	1	1
14	1	1	0	1	0	0	1	0	0	1	1
15	1	1	1	0	0	0	0	1	0	1	1
16	1	1	1	1	0	0	0	0	0	1	1

Discussions:

- The simplification by K-Map was easier
- In this case parallel circuit aren't work.

0 → 1

8 4 2 1

$$F(A, B, C, D) = \Sigma(1, 3, 9, 10, 11, 13, 15)$$

$$= A'B'C'D + A'B'CD + AB'C'D + AB'CD' + AB'CD + ABC'D + ABCD$$

	CD	$\overline{C}D'$ 00	$\overline{C}D$ 01	CD 11	CD' 10
AB					
$A'B'$ 00		0	1	3	2
$A'B$ 01		4	5	7	6
AB 11		12	13	15	14
AB' 10		8	9	11	10

$$F = AD + B'D + AB'C$$

$$= D(A+B') + AB'C$$