A decorative graphic consisting of a thin gold circle on the left and a horizontal bar with a gold-to-white gradient extending to the right. A large black left square bracket is positioned on the left side of the bar, and a large gold right square bracket is on the right side.

CSE 260

BRAC University

# Boolean Functions (Solve ?)

- Examples:

$$F1 = xyz'$$

$$F2 = x + y'z$$

$$F4 = xy' + x'z$$

$$F3 = (x'y'z) + (x'yz) + (xy')$$

x	y	z	F1	F2	F3	F4
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	1	1	1
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0

From the truth table,  $F3 = F4$ .

Can you also prove by algebraic manipulation that  $F3 = F4$ ?

SOP,  
minterm

Try it yourself: simplify the following equations


$$1. f(a,b,c,d) = abc + abd + a'bc' + cd + bd'$$

**TABLE 2-1**  
**Postulates and Theorems of Boolean Algebra**


Postulate 2	(a) $x + 0 = x$	(b) $x \cdot 1 = x$
Postulate 5	(a) $x + x' = 1$	(b) $x \cdot x' = 0$
Theorem 1	(a) $x + x = x$	(b) $x \cdot x = x$
Theorem 2	(a) $x + 1 = 1$	(b) $x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Postulate 3, commutative	(a) $x + y = y + x$	(b) $xy = yx$
Theorem 4, associative	(a) $x + (y + z) = (x + y) + z$	(b) $x(yz) = (xy)z$
Postulate 4, distributive	(a) $x(y + z) = xy + xz$	(b) $x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a) $(x + y)' = x'y'$	(b) $(xy)' = x' + y'$
Theorem 6, absorption	(a) $x + xy = x$	(b) $x(x + y) = x$

# Drawing Logic Circuit

 (ii)  $F2 = x + y'z$  (can assume that variables and their complements are available)




(iii)  $F3 = xy' + x'z$

 
 
# Analysing Logic Circuit

- When a logic circuit is provided, we can analyse the circuit to obtain the logic expression.
- Example: What is the Boolean expression of F4?



$$F4 = (A'B'+C)'$$

# Review

- If expression  $F2 = x + y'z$  is given, below is its truth table (obtained by “AND”ing  $y'$  with  $z$  and then “OR”ing the product with  $x$ .)
- So from truth table, considering the 1's we can say,  
 $F2 = x'y'z + xy'z' + xy'z + xyz' + xyz$   
which when simplified using postulates, will result to,  
 $F2 = x + y'z$

X	Y	Z	F2
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$\text{so } x + y'z = x'y'z + xy'z' + xy'z + xyz' + xyz$$

Simplified  
expression

SOP Canonical Format of the  
expression

# Review: Solve it yourself


Q1. Draw a logic circuit for  $BD + BE + D'F$

Q2. Draw a logic circuit for

$$A'BC + B'CD + BC'D + ABD'$$

# Review: Solve it yourself


- What is Boolean expression of F5?

 




# [Review: Solve it yourself]

- What is Boolean expression of  $F_2$ ?

 

# [ Review: Solve it yourself ]

- What is Boolean expression of  $F_3$ ?

 

# Standard Forms

- Two Standard Forms:  
*Sum-of-Products* and *Product-of-Sums*
- **Literals**: a variable on its own or in its complemented form. Examples:  $x$ ,  $x'$ ,  $y$ ,  $y'$
- **Product Term**: a single literal or a logical product (AND) of several literals.  
Examples:  $x$ ,  $xyz'$ ,  $A'B$ ,  $AB$

# Standard Forms

- **Sum Term**: a single literal or a logical sum (OR) of several literals.  
Examples:  $x$ ,  $x+y+z'$ ,  $A'+B$ ,  $A+B$
- **Sum-of-Products (SOP) Expression**: a product term or a logical sum (OR) of several product terms.  
Examples:  $x$ ,  $x+yz'$ ,  $xy'+x'yz$ ,  $AB+A'B'$
- **Product-of-Sums (POS) Expression**: a sum term or a logical product (AND) of several sum terms.  
Examples:  $x$ ,  $x(y+z')$ ,  $(x+y')(x'+y+z)$ ,  $(A+B)(A'+B')$
- Every boolean expression can either be expressed as sum-of-products or product-of-sums expression.

Examples:

SOP:  $x'y + xy' + xyz$

POS:  $(x + y')(x' + y)(x' + z')$

Note: SOP and POS are complements

# Minterm

- Consider two binary variables  $x$ ,  $y$ .
- Each variable may appear as itself or in complemented form as literals (i.e.  $x$ ,  $x'$  &  $y$ ,  $y'$  )
- For two variables, there are four possible combinations with the AND operator, namely:  
 $x'y'$ ,  $x'y$ ,  $xy'$ ,  $xy$
- These product terms are called the *minterms*.
- A **minterm** of  $n$  variables is the product of  $n$  literals from the different variables.
- In general,  $n$  variables can give  $2^n$  minterms.

# Maxterm

- In a similar fashion, a **maxterm** of  $n$  variables is the sum of  $n$  literals from the different variables.

Examples:  $x'+y'$ ,  $x'+y$ ,  $x+y'$ ,  $x+y$

- In general,  $n$  variables can give  $2^n$  maxterms.

# Minterm & Maxterm

- The minterms and maxterms of 2 variables are denoted by m0 to m3 and M0 to M3 respectively:

Note:

$$m_0 = x'y'z'$$

$$m_0' = xyz$$

$$M_0 = (x+y+z)$$

$$m_0' = M_0$$

Minterms				Maxterms	
x	y	term	notation	term	notation
0	0	$x'y'$	m0	$x+y$	M0
0	1	$x'y$	m1	$x+y'$	M1
1	0	$xy'$	m2	$x'+y$	M2
1	1	$xy$	m3	$x'+y'$	M3

Minterm number is the decimal representation

**Each minterm is the complement of the corresponding maxterm:**

Example:  $m_2 = xy'$

$$m_2' = (xy')' = x' + (y')' = x' + y = M_2$$

# Minterms and Maxterms

Minterms					Maxterms	
$x$	$y$	$z$	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	$m_0$	$x + y + z$	$M_0$
0	0	1	$x'y'z$	$m_1$	$x + y + z'$	$M_1$
0	1	0	$x'yz'$	$m_2$	$x + y' + z$	$M_2$
0	1	1	$x'yz$	$m_3$	$x + y' + z'$	$M_3$
1	0	0	$xy'z'$	$m_4$	$x' + y + z$	$M_4$
1	0	1	$xy'z$	$m_5$	$x' + y + z'$	$M_5$
1	1	0	$xyz'$	$m_6$	$x' + y' + z$	$M_6$
1	1	1	$xyz$	$m_7$	$x' + y' + z'$	$M_7$



# Canonical Form: Sum of Minterms

Obtain Sum-of-Minterms by gathering/summing the minterms of the function (where result is a 1)

$$F1 = xyz' = \Sigma(m6)$$

$$F2 = x'y'z + xy'z' + xy'z + xyz' + xyz = \Sigma(m1, m4, m5, m6, m7)$$

$$\begin{aligned} F3 &= x'y'z + x'yz + xy'z' \\ &\quad + xy'z \\ &= \Sigma(m1, m3, m4, m5) \end{aligned}$$

x	y	z	F1	F2	F3
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	0	0
0	1	1	0	0	1
1	0	0	0	1	1
1	0	1	0	1	1
1	1	0	1	1	0
1	1	1	0	1	0

# Canonical Form: Product of Maxterms

- Maxterms are sum terms.
- **For Boolean functions, the maxterms of a function are the terms for which the result is 0.**
- Boolean functions can be expressed as Products-of-Maxterms.

# Canonical Form: Product of Maxterms

$$\text{E.g.: } F2 = \prod(M0, M2, M3) = (x+y+z)(x+y'+z)(x+y'+z')$$

$$F3 = \prod(M0, M2, M6, M7)$$

$$= (x+y+z)(x+y'+z)(x'+y'+z)(x'+y'+z')$$

x	y	z	F1	F2	F3
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	0	0
0	1	1	0	0	1
1	0	0	0	1	1
1	0	1	0	1	1
1	1	0	1	1	0
1	1	1	0	1	0



x	y	z	Function $f_1$	Function $f_2$
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Considering the 1's ->  $f_1 = x'y'z + xy'z' + xyz' = m_1 + m_4 + m_7$   
 $= \sum (m_1, m_4, m_7)$
- Considering the 0's ->  
 $f_1' = x'y'z' + x'yz' + x'yz + xy'z + xyz' = m_0 + m_2 + m_3 + m_5 + m_6$
- $(f_1')' = f_1 = (x+y+z)(x+y'+z)(x+y'+z')(x'+y+z')(x'+y'+z)$
- $f_1 = M_0 M_1 M_2 M_5 M_6 = \prod (M_0, M_1, M_2, M_5, M_6)$

**Try writing  $f_2$  in (i) SOP and (ii) POS**

# [ Solution ]

- SOP:  $F2 = x'yz + xy'z + xyz' + xyz$
- POS:  $F2 = (x+y+z)(x+y+z')(x+y'+z)(x'+y+z)$

# Canonical Form: Product of Maxterms

- Why is this so? Take F2 as an example.

$$F2 = \Sigma(m1, m4, m5, m6, m7)$$

- The complement function of F2 is:

$$\begin{aligned} F2' &= \Sigma(m0, m2, m3) \\ &= m0 + m2 + m3 \end{aligned}$$

Therefore:

$$\begin{aligned} F2 &= (m0 + m2 + m3)' \\ &= \mathbf{m0' \cdot m2' \cdot m3'} \\ &= \mathbf{M0 \cdot M2 \cdot M3} \\ &= \Pi(M0, M2, M3) \end{aligned}$$

DeMorgan  
 $mx' = Mx$

- Every Boolean function can be expressed as either Sum-of-Minterms or Product-of-Maxterms.

x	y	z	F2	F2'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

# Comparison between SOP and POS

- **Complement of a function  
= original function-minterms  
=missing miniterms**
- $m_j' = M_j$
- If  $f(x,y,z) = \sum(1,3,6,7) = \prod(0,2,4,5)$

**Function can be expressed in both SOP and POS.**

**Step 1: interchange  $\sum$  with  $\prod$**

**Step 2: list missing numbers from the original**

# Expressing Boolean Function in terms of Canonical SOP

Check if each term contains all variable, if not  
AND  $(x+x')$  if  $x$  is the missing term

$$F=A+B'C$$

$$=A(B+B')(C+C')+B'C(A+A')$$

$$=(AB+AB')(C+C')+B'C(A+A')$$

$$=AB(C+C')+AB'(C+C')+B'C(A+A')$$

$$=ABC+ABC'+\mathbf{AB'C}+AB'C'+\mathbf{AB'C}+A'B'C$$

$$=ABC+ABC'+AB'C+AB'C'+A'B'C$$

$$=\Sigma(1,4,5,6,7)$$

Try using Truth Table



# Expressing Boolean function in terms of Canonical POS

1. Often distributive law  $(x+yz)=(x+y)(x+z)$  is used

2. If then terms, like  $x$ , are missing, OR  $xx'$

$$F = xy + x'z = (xy + x')(xy + z) = (x + x')(y + x')(x + z)(y + z) \\ = (1)(y + x')(x + z)(y + z) = (y + x')(x + z)(y + z)$$

Each POS is missing a term so OR missing terms

$$= (y + x' + zz')(x + z + yy')(y + z + xx')$$

Again applying distributive law

$$= (x + y + z)(x + y' + z)(x' + y + z)(x' + y + z') = \prod(0, 2, 4, 5)$$

Try using Truth Table

# Solving it yourself

1. A Boolean function of 5 variables can have up to \_\_\_\_\_ minterms.
2. Given a Boolean function  $F(A,B,C) = \Sigma m(0, 5, 7)$ . Which of the following is correct?
  - a)  $F'(A,B,C) = \Sigma m(0,5,7)$
  - b)  $F(A,B,C) = \Pi M(1,2,3,4,6)$
  - c)  $F(A,B,C) = \Pi M(0,5,7)$
  - d)  $F'(A,B,C) = \Sigma m(1,2,3)$
  - e) None above
3. Given a Boolean function  $F(x,y,z) = y' \cdot (x + z') + x' \cdot z$ . Which of the following is correct?
  - a)  $F(x,y,z) = \Sigma m(0,1)$
  - b)  $F(x,y,z) = \Sigma m(0,1,4,5)$
  - c)  $F(x,y,z) = \Sigma m(0,1,2,3,4)$
  - d)  $F(x,y,z) = \Sigma m(0,1,3,4,5)$
  - e)  $F(x,y,z) = \Sigma m(1,2,3,4,5)$

# [ Solution ]

- 1.  $2^5=32$
- 2. (b)
- 3.(d)

Working:

$$\begin{aligned} F(x,y,z) &= y' \cdot (x + z') + x' \cdot z = y'x + x'z \\ &= y'x(z+z') + x'z(y+y') \\ &= x'y'z' + x'y'z + x'yz + xy'z' + xy'z \\ &= m_0 + m_1 + m_3 + m_4 + m_5 \\ &= F(x,y,z) = \Sigma m(0,1,3,4,5) \end{aligned}$$



CSE260 Digital Logic Design


# Karnaugh Maps

Khadija Rasul


Aniqua Zereen
 
# [The map method]

- The map method provides a simple procedure for minimizing Boolean functions.
- The map is made up of squares where each square represent a minterm.
- We represent each minterm of an equation by '1's
- We groups the adjacent '1's in groups of 2, groups of 4 or groups of 8 and so on.
- In those grouping try to find the common literal.
- The map method is often known as Karnaugh Map or Veitech Diagram. In short we will call it K-map





(a)

 


(b)
  
# [Two variable map]

- There are 4 minterm of 2 variable; hence the map is four squares, one for each minterm.



(a)

 

(b)

# Representing function in K-map

■ (a)  $F1 = xy$ ;

		$y$	
		0	1
$x$	0		
	1		1

(a)  $xy$

■ (b)  $F2 = xy' + xy + x'y$

$$= x(y' + y) + x'y$$

$$= x + x'y$$

$$= (x + x')(x + y)$$

$$= (1)(x + y)$$

$$= x + y$$

		$y$	
		0	1
$x$	0		1
	1	1	1

(b)  $x + y$

# [ Try it yourself ]

$$F = xy' + x'y' + x'y,$$

Simplify the equation using k-map



# [ Solution ]

■  $F = xy' + x'y' + x'y = x' + y'$

		$y$	
		0	1
$x$	0	1	1
	1	1	

# [ Three variable map ]

- Sequence in 3-variable map is not in binary sequence but in reflected code. In reflected code, at a time only 1 bit changes from 0 to 1 and 1 to 0.
- Numbering of minterms follow binary numbers. Example  $m_5$  is at 101 i.e. row 1 and column 01.

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$

		yz			
		00		01	$\overbrace{11 \quad 10}^y$
x	0	000	001	011	010
$\underbrace{x}_{1}$	1	100	101	111	110
		$\underbrace{\hspace{10em}}_z$			



Note: Any 2 adjacent square differ by 1 variable ( which is primed in one and unprimed in the other )

		yz			
		00		01	$\overbrace{11 \quad 10}^y$
x	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
$\underbrace{x}_{1}$	1	$xy'z'$	$xy'z$	$xyz$	$xyz'$
		$\underbrace{\hspace{10em}}_z$			

minterms in the adjacent square are ORed, will remove the different term. As a result, we get a single ANDed term of only 2 common literals


- $F1 = \sum(5,7) = xy'z + xyz = xz(y' + y) = xz$

  - $F2 = \sum(0,2) = x'y'z' + x'yz' = x'z'(y' + y) = x'z'$


 
# Simplifying functions using k-map


- $F = \sum(2,3,4,5) = x'yz + x'yz' + xy'z' + xy'z$   
 (note: in other words,  $F = (\sum (010, 011, 100, 101))$  so place 1s in these positions and group the 1s)  
 $F = x'y + xy'$



- Grouping of 1 can be done in groups of two '1', four '1', eight '1'.... $2^n$  '1'.


■  $F1 = x'yz + xy'z' + xyz + xyz' = xz' + yz$

011      100      111      110

 

Notice even 2 opposite edges of the map are adjacent, thus they can be grouped

 - If  $F = \sum(0, 2, 4, 6)$ , then simplify it




$$\begin{aligned}
 m_0 + m_2 + m_4 + m_6 &= x'y'z' + x'yz' + xy'z' + xyz' \\
 &= x'z'(y' + y) + xz'(y' + y) \\
 &= x'z' + xz' = z'(x' + x) = z'
 \end{aligned}$$

# [ Try it yourself ]

---

- $F = \sum(0, 2, 4, 5, 6)$ , Simplify it.

# [ Solution ]

 



[ Try it yourself: ]

- $F = A'C + A'B + AB'C + BC$ 
  - a) Express it as SOP (i.e.  $\Sigma$ )
  - b) Simplify it using Kmap

# [ Solution ]

■ (a)  $F = \sum(1,2,3,5,7)$

(b)  $F = C + A'B$

	$BC$	00	01	11	10
$A$	0		1	1	1
1			1	1	

To find  $A'C$ , coincide  $A'$  (first row) with  $C$  (middle 2 column)

To find  $A'B$ , coincide  $A'$  (first row) with  $B$  (last 2 column)

To find  $BC$ , coincide  $B$  (last 2 column) with  $C$  (middle 2 column)

To find  $AB'C$ , is m5( 2<sup>nd</sup> row 2<sup>nd</sup> column)

# Summary of grouping in 3-variable map

One square represents one minterm, giving a term of three literals.

Two adjacent squares represent a term of two literals.

Four adjacent squares represent a term of one literal.

Eight adjacent squares encompass the entire map and produce a function that is always equal to 1.

		$yz$			
		00	01	11	10
$x$	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
	1	$xy'z'$	$xy'z$	$xyz$	$xyz'$

# Four variable map

- Adjacent squares can be side by side or lie in 4 corner or top-bottom or left-right edge condition. Example,  $m_0$  -  $m_2$  are adjacent and similarly  $m_3$  -  $m_{11}$  are adjacent


One square represents one minterm, giving a term of four literals.

Two adjacent squares represent a term of three literals.

Four adjacent squares represent a term of two literals.


Eight adjacent squares represent a term of one literal.

 Sixteen adjacent squares represent the function equal to 1.



- Simplify  $F = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$
- Note: it is allowed to use the same '1' more than once.

wx \ yz	00	01	11	10
00	1	1		1
01	1	1		1
11	1	1		1
10	1	1		

 

[ Try it yourself ]

■  $F = A'B'C' + B'CD' + A'BCD' + AB'C'$


$AB$	$CD$		$C$	
	00	01	11	10
00	1	1		1
01				1
11				
10	1	1		1

$A$  {  $B$  }

$D$

# [ Solution ]

■  $F = A'B'C' + B'CD' + A'BCD' + AB'C'$

 

# Product of Sum (POS) simplification

- F is represented with the '1's  
-> F' is represented with the '0's  
-> (F')' = F so find F' and then find its complement using DeMorgan's law.
- In other word, '1's represent the minterms whereas '0's represent the maxterms.
- If Equation is provided in SOP format, mark the '1's and then mark the remaining with '0's. On the other hand, if Equation is provided in POS format, mark the '0's and then mark the remaining with '1's. Once marking is done, function can be simplified in SOP or POS format.



# SOP to POS

- SOP  $\rightarrow F = \sum(0, 1, 2, 5, 8, 9, 1)$
- Combining '1's we get  
 $F = B'D' + B'C' + A'C'D$
- Combining '0's we get  
 $F' = AB + CD + BD'$
- Applying De-morgan  
 $F = (A' + B')(C' + D')(B' + D) \leftarrow \text{POS}$

AB	CD		C	
	00	01	11	10
00	1	1	0	1
01	0	1	0	0
11	0	0	0	0
10	1	1	0	1

Diagram illustrating a 4x4 Karnaugh map for a function F. The rows are labeled AB (00, 01, 11, 10) and the columns are labeled CD (00, 01, 11, 10). The map shows 1s in cells (00,00), (00,01), (01,01), (10,00), (10,01), (10,10), and (10,11). The map is grouped into three prime implicants: a 2x2 square (00,01,10,11) for  $B'D'$ , a 2x2 square (00,01,10,11) for  $B'C'$ , and a 2x2 square (00,01,10,11) for  $A'C'D$ . The map is also grouped into three prime implicants for the complement function F': a 2x2 square (00,01,10,11) for  $AB$ , a 2x2 square (00,01,10,11) for  $CD$ , and a 2x2 square (00,01,10,11) for  $BD'$ .

■ If SOP:  $\sum(1,3,4,6)$

then POS:  $\prod(0,2,5,7)$

So grouping '1's,  $F = x'z + xz'$

Grouping '0's,  $F' = xz + x'z'$   
therefore,  $F = (x' + z')(x + z)$

Truth Table of Function  $F$

$x$	$y$	$z$	$F$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

		$yz$		$y$	
		00	01	11	10
$x$	0	0	1	1	0
$x$	1	1	0	0	1
		$z$			

# [ Don't Care condition ]

- Don't cares in a Karnaugh map, or truth table, may be either **1**s or **0**s, as long as we don't care what the output is for an input condition we never expect to see.
- We plot these cells with a special sign, 'X', among the normal **1**s and **0**s.
- When forming groups of cells, treat the don't care cell as either a **1** or a **0**, or ignore the don't cares. This is helpful if it allows us to form a larger group than would otherwise be possible without the don't cares.
- There is no requirement to group all or any of the don't cares. (i.e. do not make any group only consisting the don't cares). Only use them in a group if it simplifies the logic.

Simplify  $F(w,x,y,z) = \sum(1,3,7,11,15)$  and don't care  
 $d(w,x,y,z) = \sum(0,2,5)$

Solution: Even though 2 solutions are not same, but either  
 1 is acceptable. Such scenario only applicable for Don't  
 care scenarios!

		$y$			
		$yz$			
		00	01	11	10
$w$	$wx$				
	00	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0
		$z$			

(a)  $F = yz + w'x'$

		$y$			
		$yz$			
		00	01	11	10
$w$	$wx$				
	00	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0
		$z$			

(b)  $F = yz + w'z$

# Complement of the function and POS considering don't cares

		$y$			
		$yz$			
		00	01	11	10
$w$	$wx$				
	00	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0

$x$  (grouping rows 01, 11, 10)  
 $z$  (grouping columns 01, 11)

$$F' = z' + wy'$$

$$F = (z)(w' + y)$$



# **APPLICATIONS OF K-MAP**

# Example 1: Design and draw the circuit diagram of BCD to Excess-3 code converter

BCD Input				Excess-3 Output			
B3	B2	B1	B0	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

Q1. Treat each W, X, Y and Z as a function and write them as SOP

W X  
Y Z

Q2. Based on the SOP, draw the circuit diagram of BCD to Excess-3 code converter

Any value higher than 9 will result into don't care output

┌

┐

For W

AB \ CD	00	01	11	10
00				
01		1	1	1
11	X	X	X	X
10	1	1	X	X


$$W = A + BC + BD$$

$$= A + B(C + D)$$

For Z

AB \ CD	00	01	11	10
00	1			1
01	1			1
11	X	X	X	X
10	1			X

$$Z = \bar{D}$$

 

For X

AB \ CD	00	01	11	10
00		1	1	1
01	1			
11	X	X	X	X
10		1	X	X

$$X = B\bar{C}\bar{D} + \bar{B}(C + D)$$

For Y


AB \ CD	00	01	11	10
00	1		1	
01	1		1	
11	X		X	X
10	1		X	X

$$Y = \bar{C}\bar{D} + CD$$



# Example 2: 7 segment display board

Display digit	b8	b4	b2	b1	A	B	C	D	E	F	G
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	0	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
off	1	0	1	0	0	0	0	0	0	0	0
off	1	0	1	1	0	0	0	0	0	0	0
off	1	1	0	0	0	0	0	0	0	0	0
off	1	1	0	1	0	0	0	0	0	0	0
off	1	1	1	0	0	0	0	0	0	0	0
off	1	1	1	1	0	0	0	0	0	0	0

 

┌

┐

Segment a

			!C	!C	C	C
			!D	D	D	!D
!A	!B	1	0	1	1	
!A	B	0	1	1	0	
A	B	D	D	D	D	
A	!B	1	1	D	D	

$$A + CD + B D + !B !D$$

Segment b

			!C	!C	C	C
			!D	D	D	!D
!A	!B	1	1	1	1	
!A	B	1	0	1	0	
A	B	D	D	D	D	
A	!B	1	1	D	D	

$$!B + !C !D + C D$$

Segment c

			!C	!C	C	C
			!D	D	D	!D
!A	!B	1	1	1	0	
!A	B	1	1	1	1	
A	B	D	D	D	D	
A	!B	1	1	D	D	

$$B + !C + D$$

Segment d

			!C	!C	C	C
			!D	D	D	!D
!A	!B	1	0	1	1	
!A	B	0	1	0	1	
A	B	D	D	D	D	
A	!B	1	1	D	D	

$$A + C !D + !B !D + !B C + B !C D$$

Segment e

			!C	!C	C	C
			!D	D	D	!D
!A	!B	1	0	0	1	
!A	B	0	0	0	1	
A	B	D	D	D	D	
A	!B	1	0	D	D	

$$C !D + !B !D$$

Segment f

			!C	!C	C	C
			!D	D	D	!D
!A	!B	1	0	0	0	
!A	B	1	1	0	1	
A	B	D	D	D	D	
A	!B	1	1	D	D	

$$A + B !C + !C !D + B !D$$

Segment g

			!C	!C	C	C
			!D	D	D	!D
!A	!B	0	0	1	1	
!A	B	1	1	0	1	
A	B	D	D	D	D	
A	!B	1	1	D	D	

$$A + B !C + B !D + !B C$$

# [ Try it by your self ]

- A **car garage** has a front door and one window, each of which has a sensor to detect whether it is open. A third sensor detects whether it is dark outside. A security system for the garage follows this rule: the alarm rings if the **alarm switch is turned on** and **either the front door is not closed or it is dark and the side window is not closed**.

# [Solution]

Switch On	Door	Window	Dark	AlarmRing
0	0	0	0	x
0	0	0	1	x
0	0	1	0	x
0	0	1	1	x
0	1	0	0	x
0	1	0	1	x
0	1	1	0	x
0	1	1	1	x
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

WDk

SDr

X	X	X	X
X	X	X	X
0	0	1	1
0	0	1	0

$$\text{AlarmRing} = \text{WDk} + \text{WDr}$$

Assuming

**AlarmRing** = 1 if Alarm rings, 0 otherwise.

**Switch On** = 1 if alarm switch is on, 0 otherwise.

**Door** = 1 if door is not closed, 0 otherwise.

**Window** = 1 if window is not closed.

**Dark** = 1 if it is dark outside, 0 otherwise.


[

]

# UNIVERSAL LOGIC GATES


## NAND

X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

 


## NOR

X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

 


# [ Using NAND ]


NOT Gate

 


OR Gate

 

NOT Gate

 


AND Gate

 


# [ Using NOR ]


NOT Gate

 


OR Gate

 

NOT Gate


 


AND Gate


 




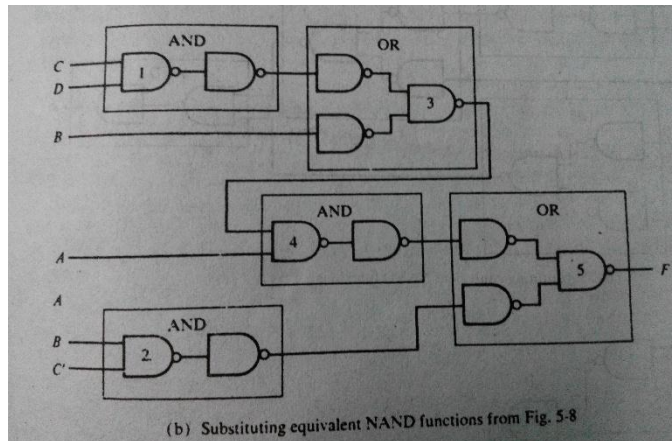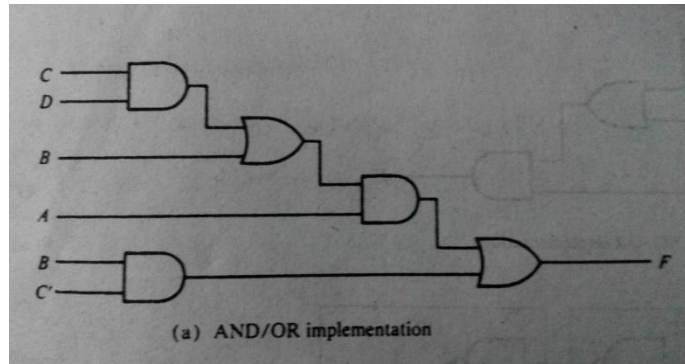Use NAND  
to  
represent  
 $F = A(B + CD) + BC'$   
+BC'



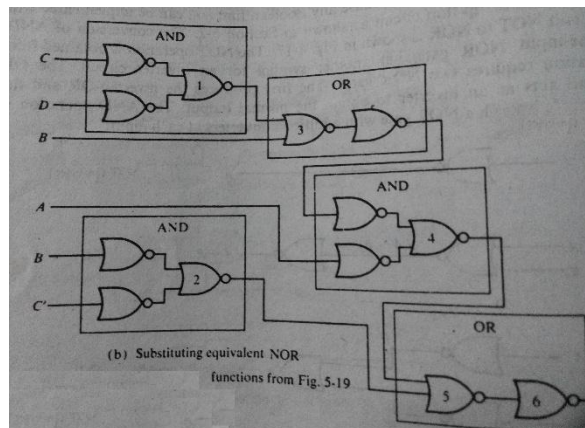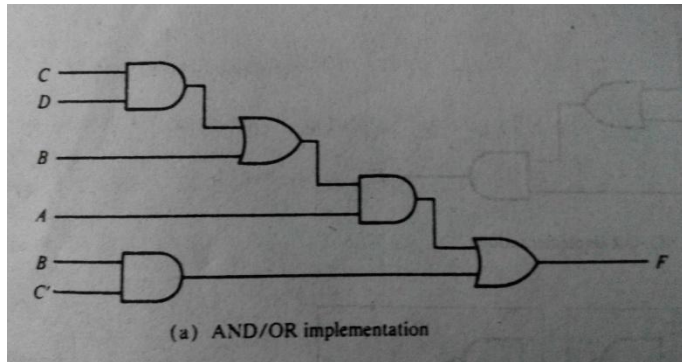Use NOR  
to  
represent  
 $F=A(B+CD)+BC'$



# [ A Must Self study from the book ]

---

- Morris Mano: Chapter 3.6 (NAND and NOR implementation )to Chapter 3.7 (Other two level implementation)