

# **CSE 260 DIGITAL LOGIC DESIGN**

## Combinational Circuits- 1


# Introduction

- Two classes of logic circuits:

- ❖ combinational

- ❖ sequential

- **Combinational Circuit:**

 

# Combinational Circuit vs. Sequential Circuit

## Combinational

- A combinational circuit consists of logic gates whose **outputs** at any time **are determined directly from the present combination of inputs** without regard to previous inputs.
- A combinational circuit **performs** a specific information-**processing** operation fully **specified** logically **by** a set **of Boolean functions**.

## Sequential


- Sequential circuits employ memory elements in addition to logic gates. **Their outputs are a function of the inputs and the state of memory elements**
- The state of memory elements, in turn, is a function of previous inputs. As a consequence, the **outputs** of a sequential circuit **depend not only on present inputs, but also on past inputs**.

- A combinational circuit consists of input variables, logic gates and output variables.
- A combinational circuit can be described by **m** Boolean functions, one for each output variable. Each output function is expressed in terms of the **n input variables**.
- There **is no feedback path** or presence of memory element

# Design Procedure:

The design of combinational circuits starts from the verbal outline of the problem and ends in a logic circuit diagram.

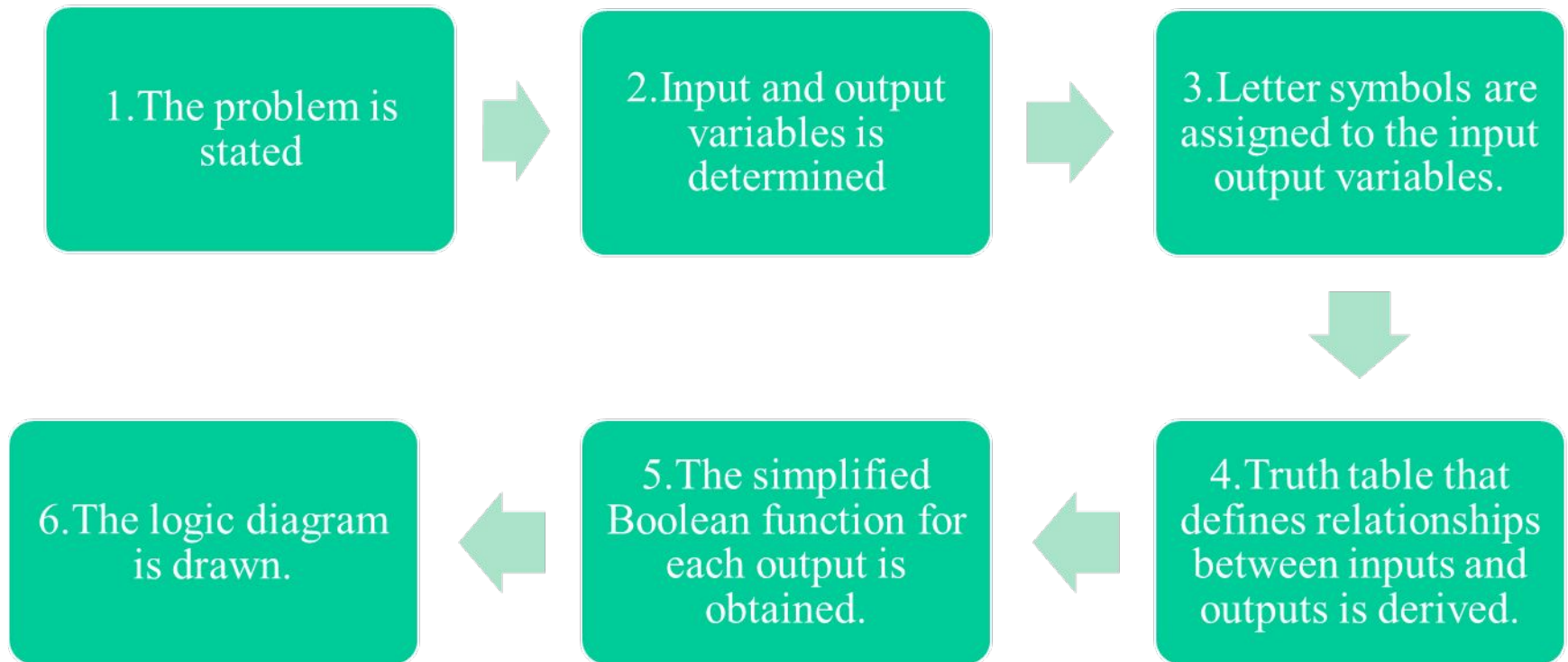
**The procedure involves the following steps:**



*Hint: Aren't these the steps used for solving car-garage alarm system?!!!! So we are familiar with combinational circuit design! 😊*
 
# Design Procedure: Half Adder

- The combinational circuit that performs the addition of two bits is called a half-adder.
- 1) State Problem  
Example: Build a **Half Adder** to add two bits
- 2) Determine and label the inputs & outputs of circuit.  
Example: Two inputs and two outputs labeled, as follows:



- 3) Draw truth table.

# Design Procedure: Half Adder

4) Obtain simplified Boolean function.

Example:  $C = XY$

$$S = X'Y + XY' = X \oplus Y$$

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

5) Draw logic diagram.


Half Adder

# Ways to draw half-adder

- Method 1:

$$S = xy' + x'y$$

$$C = xy$$

 

(a)  $S = xy' + x'y$   
 $C = xy$




# Ways to draw half-adder

- Method 2:

$$S = xy' + x'y = (x + y)(x' + y') \text{ (i.e. POS format)}$$

$$C = xy$$

 

$$(b) \quad S = (x + y)(x' + y') \\ C = xy$$


# Ways to draw half-adder

- Method 3:

$$S = xy' + x'y$$

$$S = (S')' = (xy + x'y')' \\ = (C + x'y')'$$

$$C = xy$$

 

(c)  $S = (C + x'y')'$   
 $C = xy$


# Ways to draw half-adder

- Method 4:

$$S = xy' + x'y$$

$$= (x + y)(x' + y')$$
 
$$C = (C')' = ((xy)')'$$
$$= (x' + y')'$$



(d)  $S = (x + y)(x' + y')$   
 $C = (x' + y')'$


# Ways to draw half-adder

- Most commonly used

$$S = xy' + x'y$$

$$= x \oplus y$$

$$C = xy$$

 

(e)  $S = x \oplus y$   
 $C = xy$


# Design Procedure : Full Addder

- Half-adder adds up only two bits.
- To add two binary numbers, we need to add 3 bits (including the *carry*).

■ Example:

	1	1	1		carry
	0	0	1	1	X
+	0	1	1	1	Y
<hr/>					
	1	0	1	0	S
<hr/>					

 - Need **Full Addder** (so called as it can be made from two half-adders).



# Design Procedure : Full Adder

- Truth table:

$x$	$y$	$z$	$C$	$s$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Note:

Z - carry in (to the current position)


C - carry out (to the next position)

- From truth table


$$C = X'YZ + XY'Z + XYZ' + XYZ$$

$$S = X'Y'Z + XYZ + X'YZ' + XY'Z'$$

# Design Procedure : Full Adder

 

$$S = x'y'z + x'yz' + xy'z' + xyz$$

 

$$C = xy + xz + yz$$

**FIGURE 4-3**

Maps for a full-adder

- Alternative formulae using algebraic manipulation, Using K-map, simplified SOP form:

$$C = XY + XZ + YZ$$

$$S = X'Y'Z + XYZ + X'YZ' + XY'Z'$$

# Gate-level (SSI) Design: Full Adder

$$\begin{aligned}C &= XY + XZ + YZ \\&= XY + (X + Y)Z \\&= XY + ((X \oplus Y) + XY)Z \\&= XY + (X \oplus Y)Z + XYZ \\&= XY + (X \oplus Y)Z\end{aligned}$$

$$\begin{aligned}S &= X'Y'Z + X'YZ' + XY'Z' + XYZ \\&= X'(Y'Z + YZ') + X(Y'Z' + YZ) \\&= X'(Y \oplus Z) + X(Y \oplus Z)' \\&= X \oplus (Y \oplus Z) \quad \text{or} \quad (X \oplus Y) \oplus Z\end{aligned}$$

Note:

How to turn  $(X+Y)$  to  $((X \oplus Y) + XY)$

If  $F=(X+Y)$

$$=(X+Y)(Y+Y')$$

$$=XY+XY'+YY+YY'$$

$$=XY+XY'+Y$$

$$=XY'+XY+Y$$

$$=XY'+Y(X+1)$$

$$=XY'+Y$$

$$=XY'+Y(X'+X)$$

$$=XY'+X'Y+XY$$

$$=(X \oplus Y) + XY$$




# Gate-level (SSI) Design: Full Adder

- Circuit for above formulae:

$$C = XY + (X \oplus Y)Z$$

$$S = (X \oplus Y) \oplus Z$$

 

Full Adder made from two Half-Adders (+ OR gate).

# Design Methods

- Different combinational circuit design methods:
  - ❖ Gate-level method (with logic gates)
  - ❖ Block-level design method
- Design methods make use of logic gates and useful functional blocks.
  - ❖ These are available as Integrated Circuit (IC) chips.

# Why is it better to use IC than classical gate method?

- IC consists of gates all packed up together internally, which keeps the gates safe inside as well as makes it economical by reducing external interconnection wires
- As number of input increase, making the truth table and k-map gets cumbersome

# Design Methods

- Type of IC chips (based on packing density) :
  - ❖ Small-scale integration (SSI): up to 12 gates
  - ❖ Medium-scale integration (MSI): 12-99 gates
  - ❖ Large-scale integration (LSI): 100-9999 gates
  - ❖ Very large-scale integration (VLSI): 10,000-99,999 gates
  - ❖ Ultra large-scale integration (ULSI): > 100,000 gates
- *Main objectives of circuit design:*
  - ❖ (i) reduce cost
    - reduce number of gates (for SSI circuits)
    - reduce IC packages (for complex circuits)
  - ❖ (ii) increase speed
  - ❖ (iii) design simplicity (reuse blocks where possible)

# Block-Level Design Method

- More complex circuits can be built using block-level method.
- In general, block-level design method (as opposed to gate-level design) relies on algorithms or formulae of the circuit, which are obtained by **decomposing the main problem to sub-problems** recursively (until small enough to be directly solved by blocks of circuits).


# What if we want to add more than 3 bit?

N-bit Full adder Can be

- Series adder: consist of 1 full adder and a storage for saving Carry out (which becomes Carry in for next bits addition)
- Parallel adder: Consist of n adder and all n-bits of both number are given as input simultaneously. Carry input, in the least significant position, must be 0.
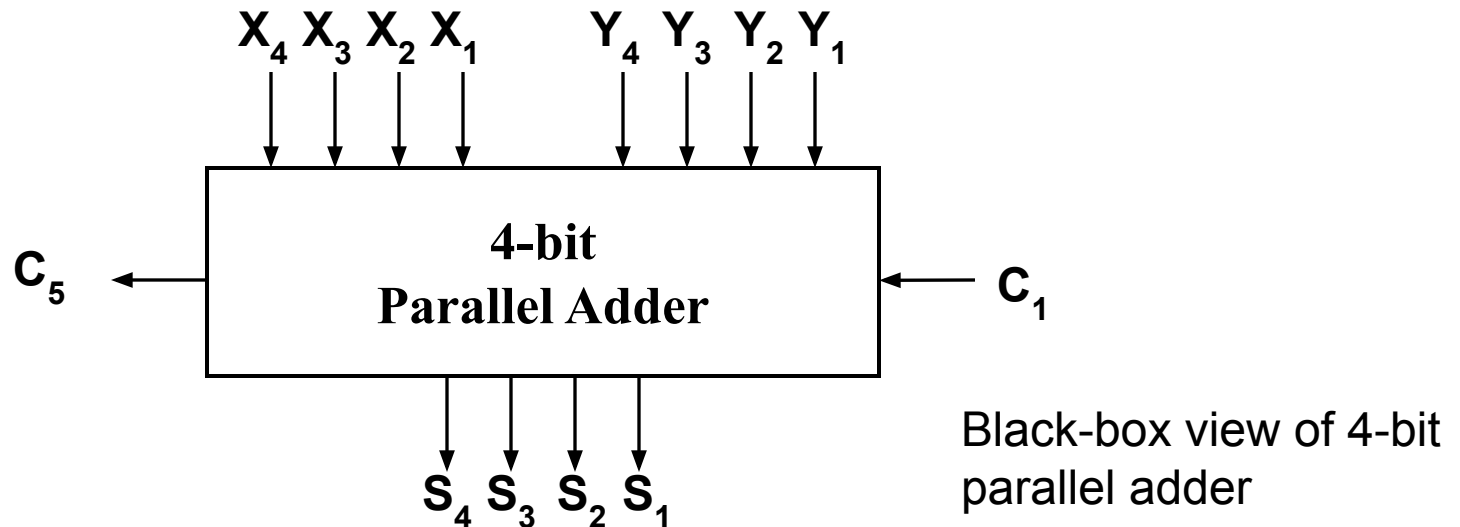
# 4-bit Parallel Adder

- Consider a circuit to add two 4-bit numbers together and a carry-in, to produce a 5-bit result:



- 5-bit result is sufficient because the largest result is:

$$(1111)_2 + (1111)_2 + (1)_2 = (11111)_2$$

# 4-bit Parallel Adder

- SSI design technique should not be used.
- Truth table for 9 inputs very big, i.e.  $2^9=512$  entries:

$X_4X_3X_2X_1$	$Y_4Y_3Y_2Y_1$	$C_1$	$C_5$	$S_4S_3S_2S_1$
0 0 0 0	0 0 0 0	0	0	0 0 0 0
0 0 0 0	0 0 0 0	1	0	0 0 0 1
0 0 0 0	0 0 0 1	0	0	0 0 0 1
...	...	...	...	...
0 1 0 1	1 1 0 1	1	1	0 0 1 1
...	...	...	...	...
1 1 1 1	1 1 1 1	1	1	1 1 1 1

- Simplification very complicated as no. of input is 9 so  $512(=2^9)$  possible combination will be there in truth table!



# 4-bit Parallel Adder

- Alternative design possible.
- Addition formulae for each pair of bits (with carry in).

output

$$C_{i+1} S_i = X_i + Y_i + C_i$$

input

has the same function as a full adder.

$$C_{i+1} = X_i Y_i + (X_i \oplus Y_i) C_i$$

$$S_i = X_i \oplus Y_i \oplus C_i$$



NB: Similar to FA equation

$$C = XY + (X \oplus Y)Z$$

$$S = (X \oplus Y) \oplus Z$$
 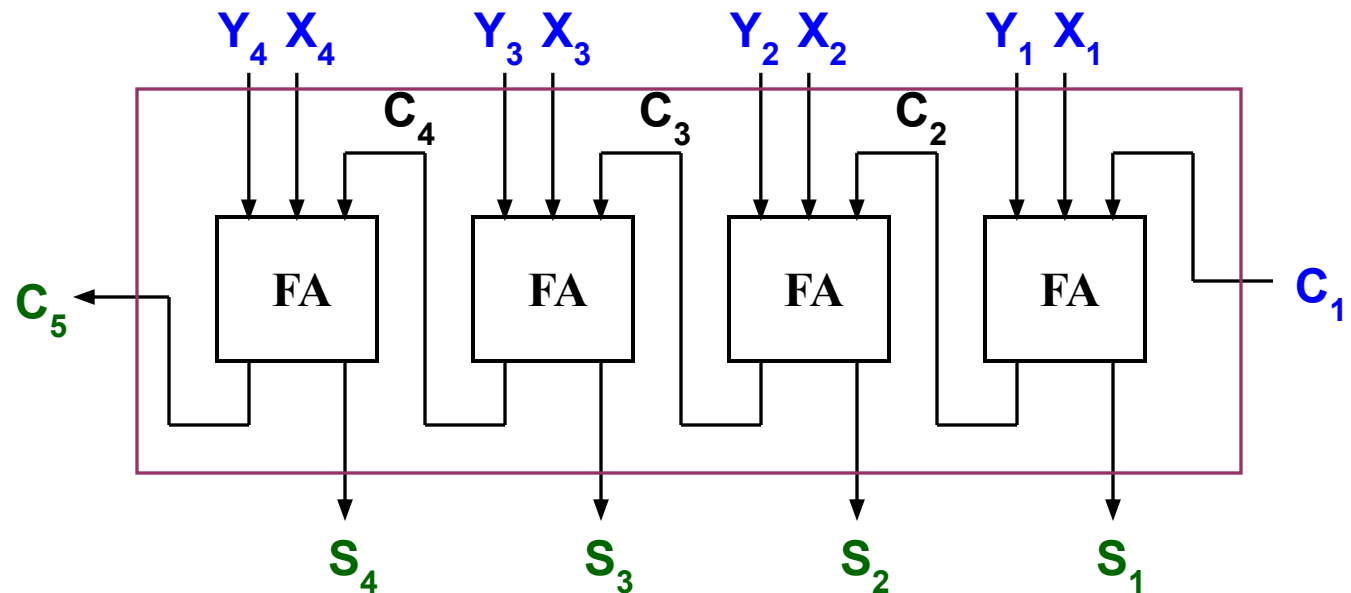
# 4-bit Parallel Adder

- Cascading 4 full adders via their carries, we get:




$n$ -bit full adder requires  $n$  full- adders

# Examples

- Simple examples using 4-bit parallel adder as building blocks:
  - ❖ 16-Bit Parallel Adder
  - ❖ Adder cum Subtractor
  - ❖ BCD to excess 3 code converter
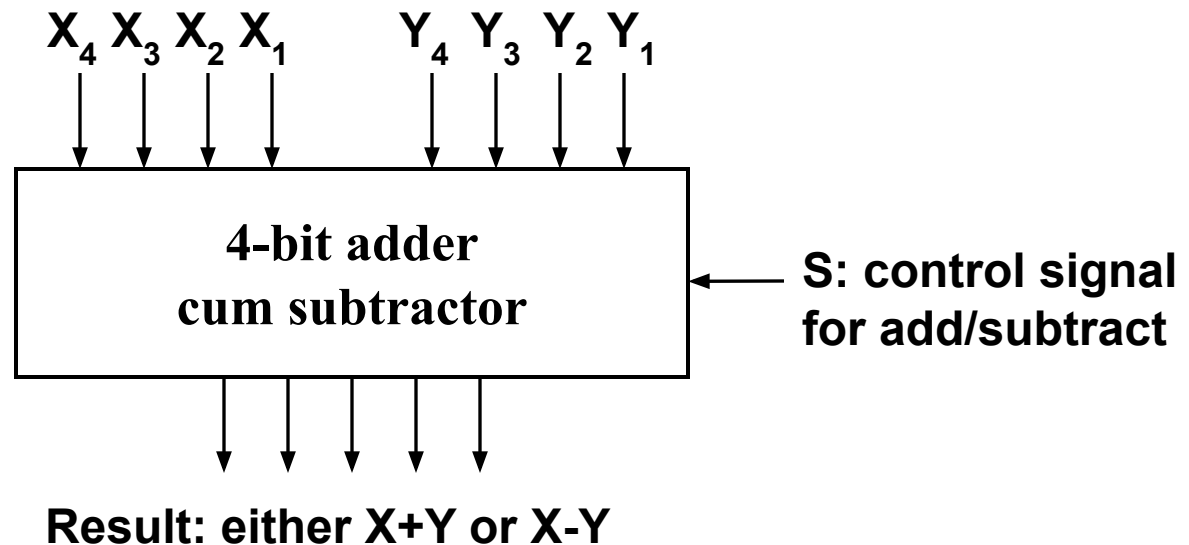
# 4-bit Parallel Adder cum Subtractor

- Subtraction can be performed through addition using 2s-complement numbers.
- Hence, we can design a circuit which can perform **both addition and subtraction**, using a parallel adder.



# 4-bit Parallel Adder cum Subtractor

- The control signal  $S=0$  means add  
 $S=1$  means subtract

- Recall that:

$$X - Y = X + (-Y)$$

$$= X + \text{(2's complement of Y)}$$



$$= X + \text{(1's complement of Y)} + 1$$

$$X + Y = X + (Y)$$

# 4-bit Parallel Adder cum Subtractor

- Design requires:

(i) XOR gates:

  


such that: output = Y when S=0  
= Y' when S=1

(ii) S connected to carry-in.

S	Y	Output
0	0	0
0	1	1
1	0	1
1	1	0

# 4-bit Parallel Adder cum Subtractor

- Adder cum subtractor circuit:

 

*Analysis:*

If  $S=1$ , then


$X + (1\text{'s complement of } Y) + 1$   
appears as the result.

If  $S=0$ , then  $X+Y$  appears as  
the result.

A 4-bit adder cum subtractor
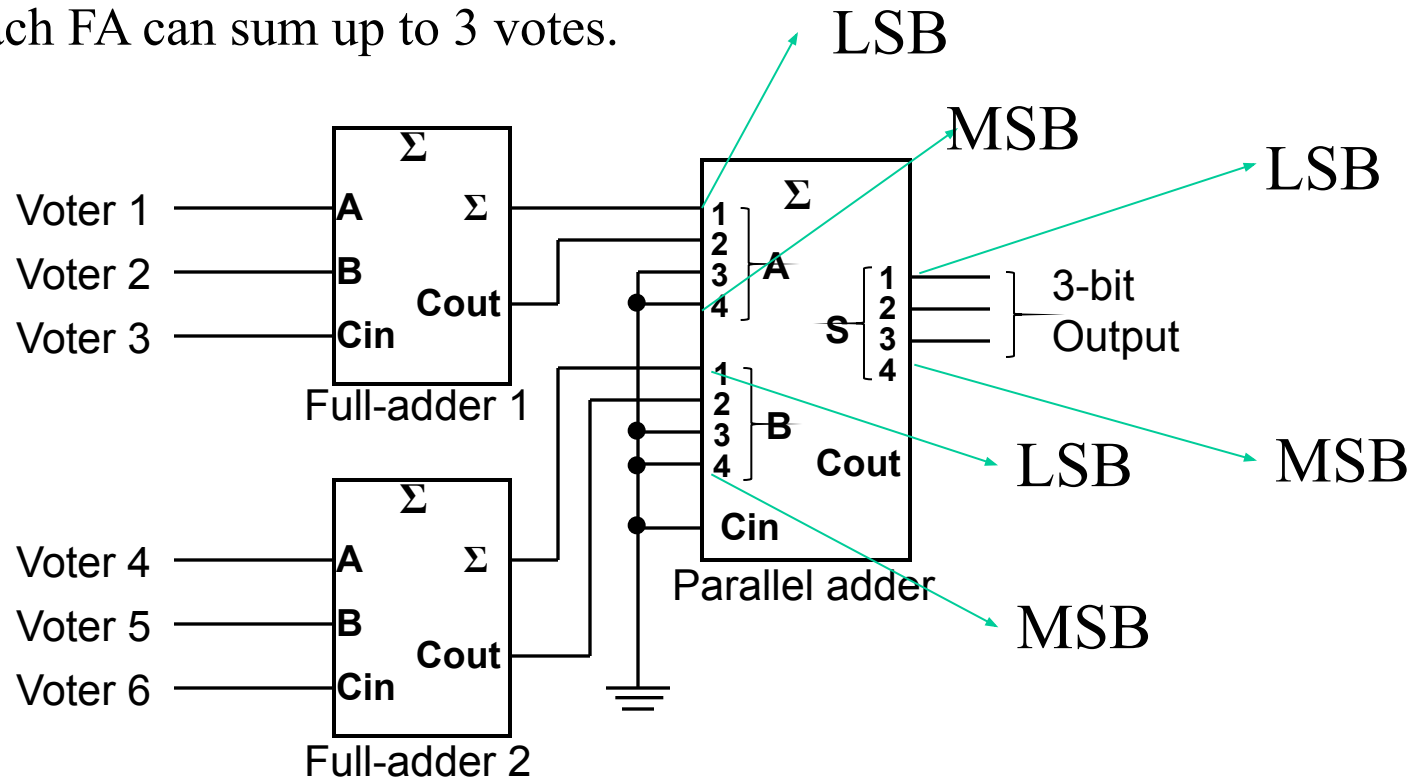
# Arithmetic Circuits: Cascading Adders

- Application: 6-person voting system.
  - ❖ Use FAs and a 4-bit binary parallel adder.
  - ❖ Each FA can sum up to 3 votes.






# Try it yourself


- Design a 12 person voting system

# Solution

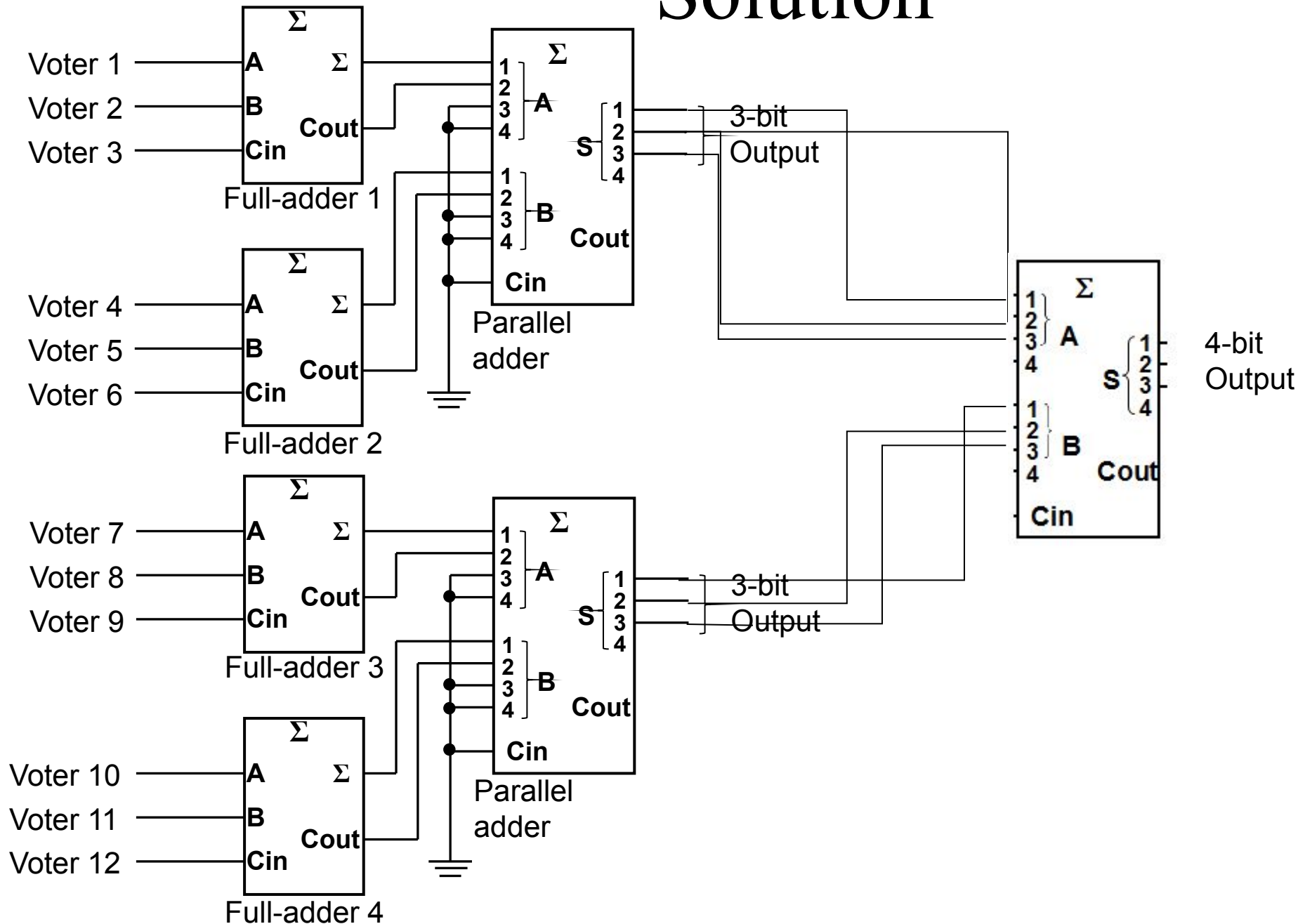
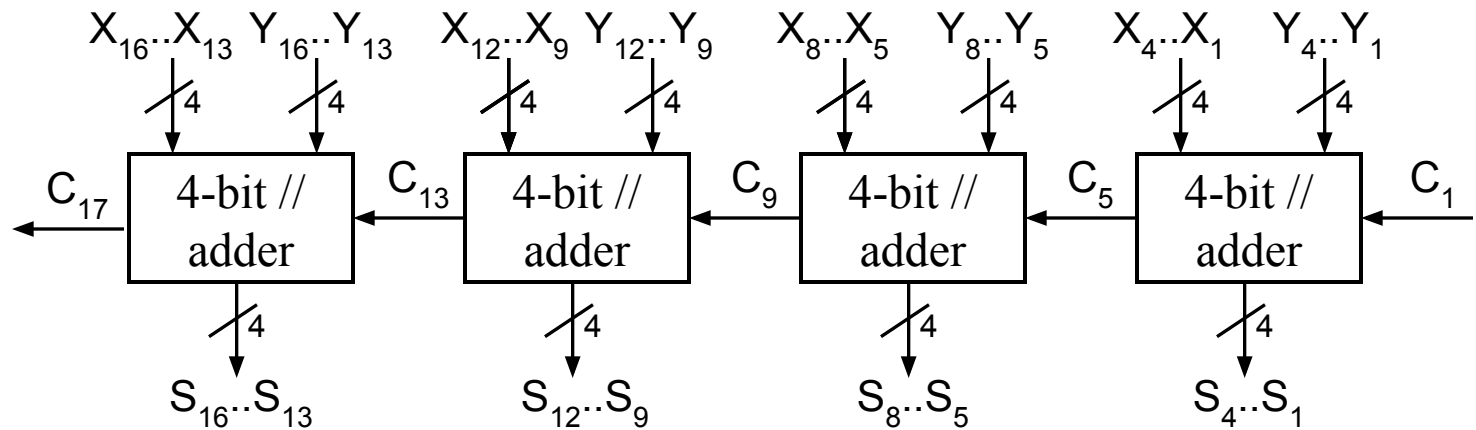
# 16-bit Parallel Adder


- Larger parallel adders can be built from smaller ones.
- Example: a **16-bit parallel adder** can be constructed from four 4-bit parallel adders:



A 16-bit parallel adder

# 16-bit Parallel Adder

- Shortened notation for multiple lines.

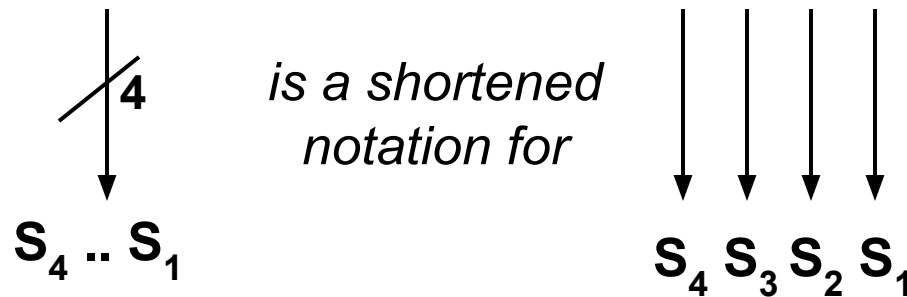


16-bit parallel adder ripples carry from one 4-bit block to the next.

Such ripple-carry circuits are “slow” because of long delays needed to propagate the carries.

# Try it yourself

- BCD to excess 3 code converter using **4-bit Parallel adder**


# BCD to excess 3 code converter

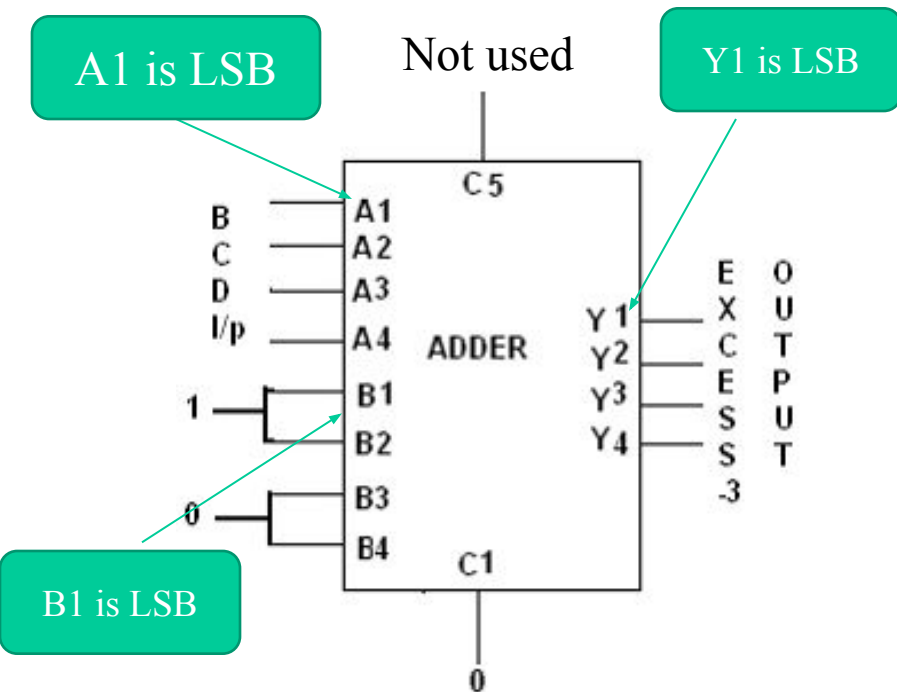

Inspection of truth table of 'excess 3 from bcd' shows that we can get excess-3 code from bcd by adding '0011' to each BCD number. This addition can be implemented by means of 4-bti full adder MSI circuit.
 
# Code Converters

- Code converters – take an input code, translate to its equivalent output code.



- Example: **BCD to Excess-3 Code Converter.**

*Input:* BCD digit



*Output:* Excess-3 digit

# Propagation Delay


- Every logic gate experiences some delay (though very small) in propagating signals forward.
- This delay is called **Gate (Propagation) Delay**.
- Formally, it is the average transition time taken for the output signal of the gate to change in response to changes in the input signals.
- **Three different propagation** delay times associated with a logic gate:
  - ❖  $t_{\text{PHL}}$ : output changing from the High level to Low level
  - ❖  $t_{\text{PLH}}$ : output changing from the Low level to High level
  - ❖  $t_{\text{PD}} = (t_{\text{PLH}} + t_{\text{PHL}})/2$  (average propagation delay)




# Propagation Delay

  


# Propagation Delay

 

- Ideally, no delay:

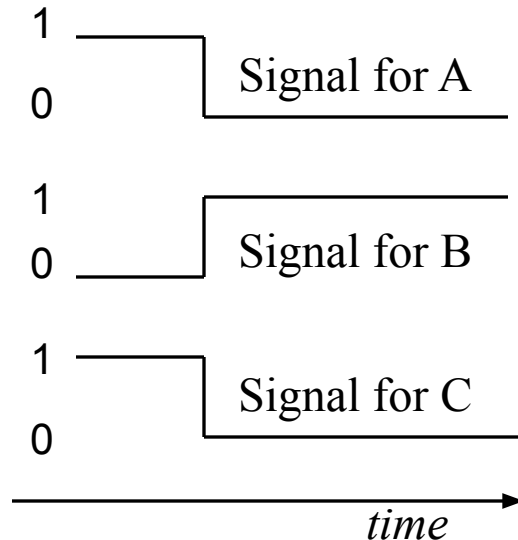


 - In reality, output signals normally lag behind input signals:


 
# Calculation of Circuit Delays

- In general, given a logic gate with delay,  $t$ .




If inputs are stable at times  $t_1, t_2, \dots, t_n$ , respectively; then the earliest time in which the output will be stable is:

$$\max(t_1, t_2, \dots, t_n) + t$$

- To calculate the delays of all outputs of a combinational circuit, repeat above rule for all gates.
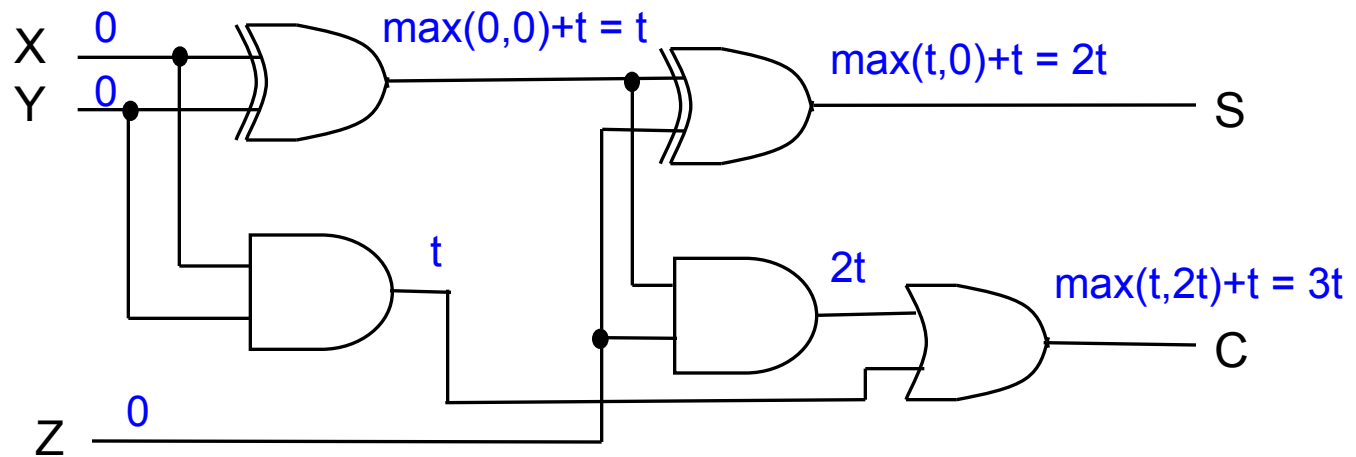
# Calculation of Circuit Delays


- As a simple example, consider the full adder circuit where all inputs are available at time 0. (Assume each gate has delay  $t$ .)



where outputs **S** and **C**, experience delays of  $2t$  and  $3t$ , respectively.
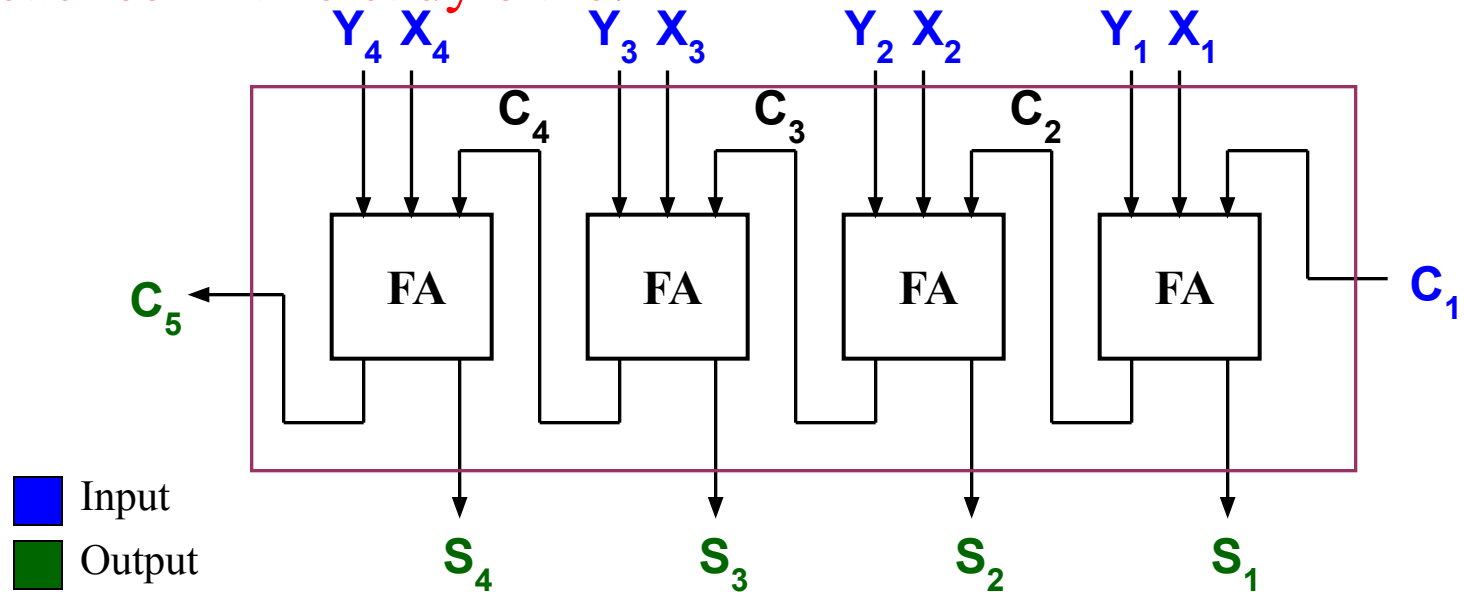
# 4-bit Parallel Adder

- Propagation time = no. of gates \* propagation delay of each gate.
- Longest propagation delay is equal to carry to propagate through all 4 full adder. **Only after the arrival of carry,  $S_4$  and  $C_5$  reaches final steady state.**



$n$ -bit full adder requires  $n$  full- adders

# HomeWork for next class

- Obtain a NAND logic diagram of a single full-adder from the Boolean functions:
  - \*  $C = xy + xz + yz$
  - \*  $S = C'(x + y + z) + xyz$

# A Must Self study

- ‘Chapter 4.9 : Exclusive OR and Equivalence Function’ (page 145 to page 149) of Morris Mano