



CSE 260

BRAC University



Theorem and Postulate

- Postulates are assumed to be true and we need not prove them. They provide the starting point for the proof of a theorem.
- A theorem is a proposition that can be deduced from postulates. We make a series of logical arguments using these postulates to prove a theorem.

Binary Logic

- Binary logic consists of binary variables and logical operations.
- Variables are designated by letters such as A, B, C, x, y, z etc. with only 2 possible values: 1 and 0.
- Logic operations: and, or, not etc.

Logic Gates

- The most basic digital devices are called gates.
- A gate has one or more inputs and produces an output that is a function of the current input values.

Most Important logic gates


- AND
- OR
- NOT

2-input AND gate



A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

2- input OR gate

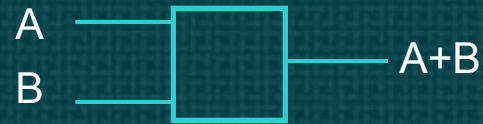

A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1

NOT gate (Inverter)



A	A'
0	1
1	0


Some Other Gates

- NAND
- NOR
- XOR
- XNOR (equivalence)

2-input NAND gate



A	B	$(A.B)'$
0	0	1
0	1	1
1	0	1
1	1	0

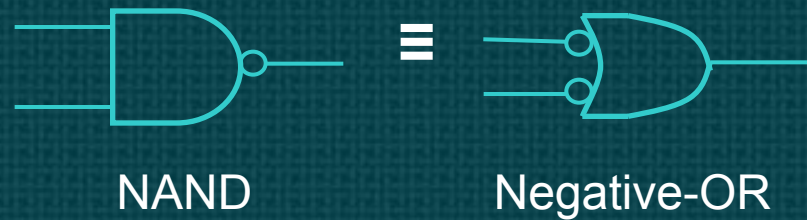

2-input NOR gate



A	B	$(A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0



NOR

\equiv



Negative-AND

2-input XOR gate



A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

2-input XNOR gate




A	B	$A \oplus B$
0	0	1
0	1	0
1	0	0
1	1	1

Universal gates


NAND

X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

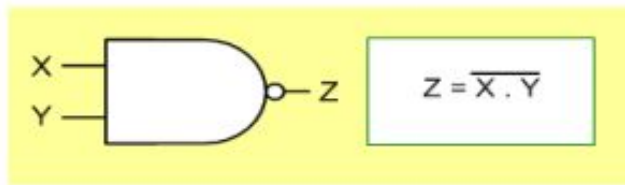

NOR


X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

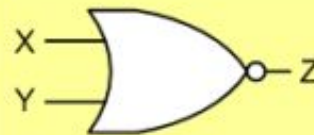


$$Z = \overline{X + Y}$$

Using NAND


NOT Gate

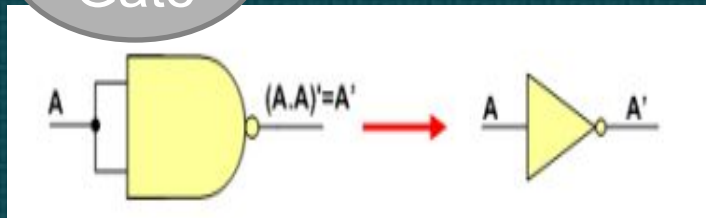


OR Gate

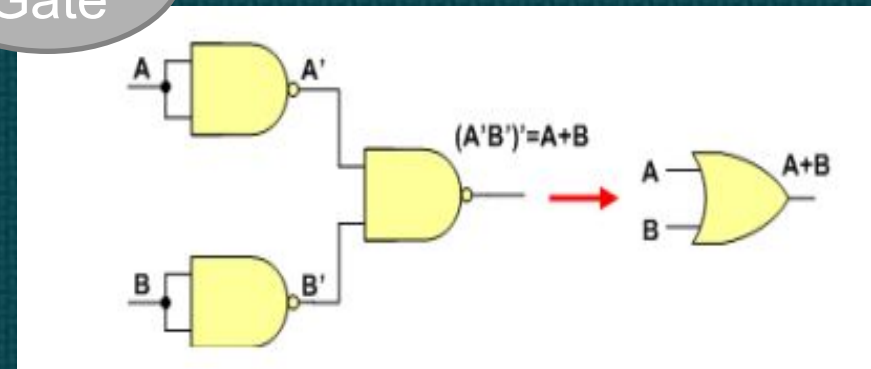

NOT Gate

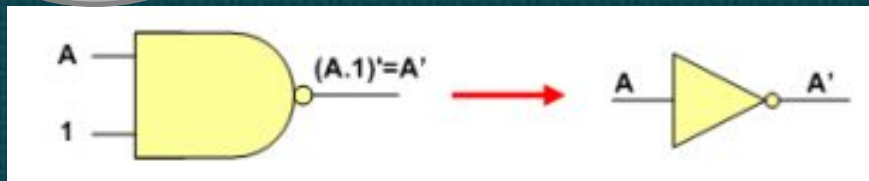


AND Gate

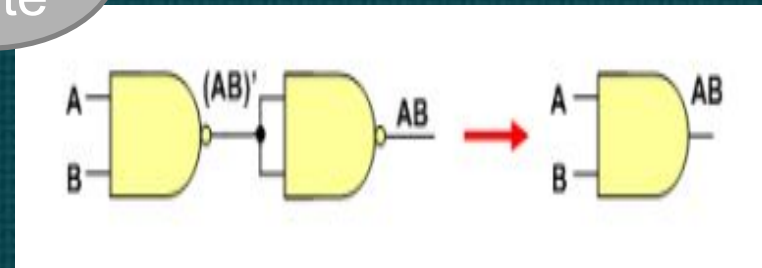


Using NOR


NOT Gate

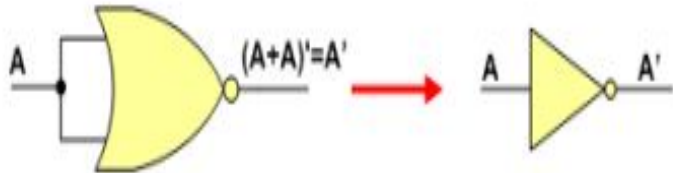


OR Gate

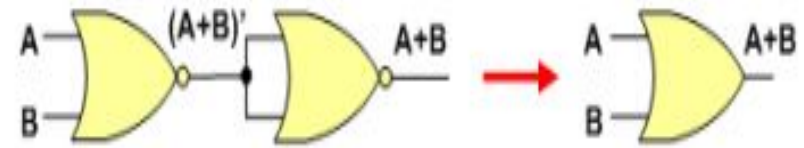

NOT Gate

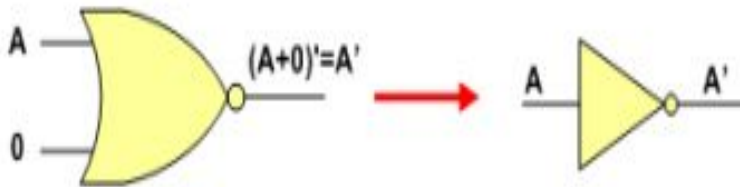

AND Gate

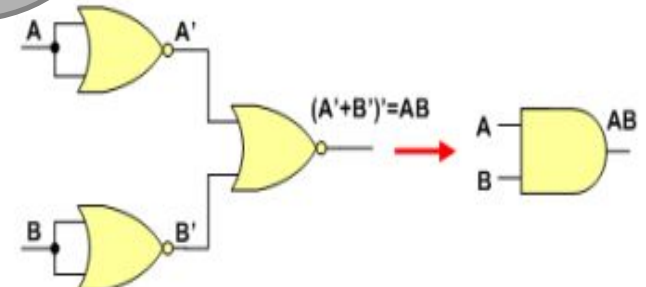

Truth Table

- Provides a listing of every possible combination of inputs and its corresponding outputs.

INPUTS	OUTPUTS
...	...
...	...

- Example (2 inputs, 2 outputs):

x	y	$x \cdot y$	$x + y$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

Proof using Truth Table

■ Prove that: $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$

(i) Construct truth table for LHS & RHS of above equality.

Note: if there are 3 variable, truth table should have 2^n combination of input

x	y	z	$y + z$	$x \cdot (y + z)$	$x \cdot y$	$x \cdot z$	$(x \cdot y) + (x \cdot z)$
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

(ii) Check that LHS = RHS

Postulate is SATISFIED because output column 5 & 8 (for LHS & RHS expressions) are equal for all cases.



BOOLEAN ALGEBRA



Boolean Algebra

- Like any other deductive mathematical system, defined with a set of elements, a set of operators and a number of axioms or postulates.
- In Boolean algebra, set consists at least 2 variables say x & y , with 2 binary operations $\{+\}$ and $\{.\}$ and 1 unary operation $\{ '\}$

Boolean algebra Postulates

- **Closure:** For every x, y in B [let, B is the set],
 - ❖ $x + y$ is in B
 - ❖ $x \cdot y$ is in B
- **Commutative laws:** For every x, y in B ,
 - ❖ $x + y = y + x$
 - ❖ $x \cdot y = y \cdot x$
- **Complement:** For every x in B , there exists an element x' in B such that
 - ❖ $x + x' = 1$
 - ❖ $x \cdot x' = 0$

Boolean algebra Postulates

- **Associative laws:** For every x, y, z in B ,
 - ❖ $(x + y) + z = x + (y + z) = x + y + z$
 - ❖ $(x \cdot y) \cdot z = x \cdot (y \cdot z) = x \cdot y \cdot z$
- **Identities** (0 and 1):
 - ❖ $0 + x = x + 0 = x$ for every x in B
 - ❖ $1 \cdot x = x \cdot 1 = x$ for every x in B
- **Distributive laws:** For every x, y, z in B ,
 - ❖ $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$
 - ❖ $x + (y \cdot z) = (x + y) \cdot (x + z)$

Duality

- **Duality Principle** – every valid Boolean expression (equality) remains valid if the operators and identity elements are interchanged, as follows:

$$+ \leftrightarrow \cdot$$

$$1 \leftrightarrow 0$$

- Example: Given the expression

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

then its dual expression is

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

Duality

- Duality gives free theorems – “two for the price of one”. You prove one theorem and the other comes for free!

- If $(x+y+z)' = x'.y'.z'$ is valid, then its dual is also valid:

$$(x.y.z)' = x'+y'+z'$$

- If $x + 1 = 1$ is valid, then its dual is also valid:

$$x . 0 = 0$$

Basic Theorems of Boolean Algebra

- Postulate 5 (a) $x+0=x$ (b) $x.1=x$ **identity**
- Postulate 3 (a) $x+x'=1$ (b) $x.x'=0$ **complement**
- Th 1 (a) $x+x=x$ (b) $x.x=x$
- Th 2 (a) $x+1=1$ (b) $x.0=0$
- Th 3, involution $(x')'=x$
- Pos 2 (a) $x+y=y+x$ (b) $xy=yx$ **commutative**
- Th 4 (a) $x(yz)=(xy)z$ (b) $x+(y+z)=(x+y)+z$
- Pos 6 (a) $x(y+z)=xy+xz$ (b) $x+yz=(x+y)(x+z)$ **Distributive**
- Th 5, DeMorgan (a) $(x+y)'=x'y'$ (b) $(xy)'=x'+y'$ **-ve**
- Th 6, Absorption (a) $x+xy=x$ (b) $x(x+y)=x$

All are very very important!

Basic Theorems of Boolean Algebra

- Theorems can be proved using **the truth table** method. (Exercise: Prove De-Morgan's theorem using the truth table.)
- They can also be proved by **algebraic manipulation** using axioms/postulates or other basic theorems.

- Theorem 2a can be proved by:

$$\begin{aligned}x + 1 &= x + (x + x') \text{ (complement)} \\&= (x + x) + x' \text{ (Th. 4)} \\&= x + x' \text{ (complement)} \\&= 1\end{aligned}$$

- By duality, theorem 2b:

$$x.(0) = 0$$

- *Note: There can be other ways of making this proof.
See Morris Mano*

Basic Theorems of Boolean Algebra

- Theorem 6a (absorption) can be proved by:

$$\begin{aligned}x + x.y &= x.1 + x.y && \text{(identity)} \\&= x.(1 + y) && \text{(distributivity)} \\&= x.(y + 1) && \text{(commutativity)} \\&= x.1 && \text{(Theorem 2a)} \\&= x && \text{(identity)}\end{aligned}$$


- By duality, theorem 6b:

$$x.(x+y) = x$$

- Try prove this by algebraic manipulation.

Operator Precedence

- Parenthesis
- NOT
- AND
- OR

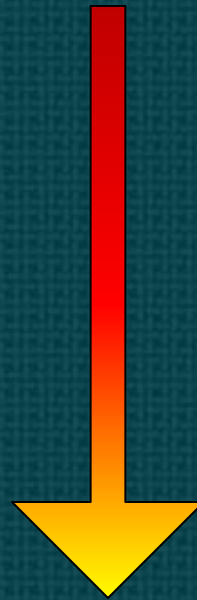


Highest


Lowest

Venn Diagram

- ven diagram for boolean algebra

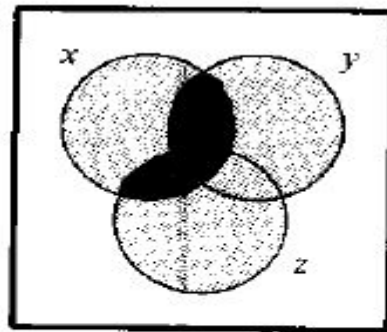

$$x(y + z)$$

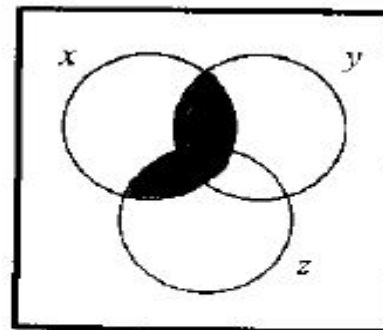

$$xy + xz$$

FIGURE 2-3

Venn diagram illustration of the distributive law

Boolean Functions (Solve ?)

- Examples:

$$F1 = xyz'$$

$$F2 = x + y'z$$

$$F3 = (x'y'z) + (x'yz) + (xy')$$

$$F4 = xy' + x'z$$

x	y	z	F1	F2	F3	F4
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	1	1	1
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0

From the truth table, $F3 = F4$.

Can you also prove by algebraic manipulation that $F3 = F4$?

- $F3 = (x'y'z) + (x'yz) + (xy')$
 $= x'y'z + x'yz + xy'$
 $= x'z(y' + y) + xy'$
 $= x'z(1) + xy'$
 $= x'z + xy'$
 $= F4$

Try it yourself

a) Simplify to minimum literals: $xy + xy'$

b) Reduce to 4 literals (variables):

$$BC + AC' + AB + BCD$$

TABLE 2-1
Postulates and Theorems of Boolean Algebra

Postulate 2	(a) $x + 0 = x$	(b) $x \cdot 1 = x$
Postulate 5	(a) $x + x' = 1$	(b) $x \cdot x' = 0$
Theorem 1	(a) $x + x = x$	(b) $x \cdot x = x$
Theorem 2	(a) $x + 1 = 1$	(b) $x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Postulate 3, commutative	(a) $x + y = y + x$	(b) $xy = yx$
Theorem 4, associative	(a) $x + (y + z) = (x + y) + z$	(b) $x(yz) = (xy)z$
Postulate 4, distributive	(a) $x(y + z) = xy + xz$	(b) $x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a) $(x + y)' = x'y'$	(b) $(xy)' = x' + y'$
Theorem 6, absorption	(a) $x + xy = x$	(b) $x(x + y) = x$

Solution

- A) $xy + xy' = x(y + y') = x(1) = x$
- B) $BC + AC' + AB + BCD$
 $= BC(1 + D) + AC' + AB$
 $= BC(1) + AC' + AB$
 $= BC + AB + AC'$
 $= B(C + A) + AC'$

Try it yourself: simplify the following equations

1. $x+x'y$

2. $x(x'+y)$

3. $x'y'z+x'yz+xy'$

TABLE 2-1

Postulates and Theorems of Boolean Algebra

Postulate 2	(a) $x + 0 = x$	(b) $x \cdot 1 = x$
Postulate 5	(a) $x + x' = 1$	(b) $x \cdot x' = 0$
Theorem 1	(a) $x + x = x$	(b) $x \cdot x = x$
Theorem 2	(a) $x + 1 = 1$	(b) $x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Postulate 3, commutative	(a) $x + y = y + x$	(b) $xy = yx$
Theorem 4, associative	(a) $x + (y + z) = (x + y) + z$	(b) $x(yz) = (xy)z$
Postulate 4, distributive	(a) $x(y + z) = xy + xz$	(b) $x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a) $(x + y)' = x'y'$	(b) $(xy)' = x' + y'$
Theorem 6, absorption	(a) $x + xy = x$	(b) $x(x + y) = x$

Solution

$$1. x+x'y=(x+x').(x+y)=1.(x+y)=x+y$$

$$2. x(x'+y)=xx'+xy=0+xy=xy$$

$$3. x'y'z+x'yz+xy' = \\ x'z(y'+y)+xy'=x'z+xy'$$

Now Try Proving Using Truth Table!!!

Complementing a function

1. Take dual of the function
2. Complement each literals

Example: $F1 = x'yz' + x'y'z$

1. Dual of the function F1 is
 $(x' + y + z')(x' + y' + z)$
2. Complement each literal =
 $(x + y' + z)(x + y + z')$

Therefore, $F1' = (x + y' + z)(x + y + z')$



Same as
applying
De-Morgan's
law on the
function

Try it urself

- What is the complement of $F2 = x(y'z' + yz)$

Solution

- $F2' = (x(y'z' + yz))'$
- Duality: $x + (y' + z')(y + z)$
- Complement = $x' + (y' + z')(y + z)$

Therefore $F2' = x' + (y + z)(y' + z')$

More Practice:

Simplify the following Boolean expression to a minimum number literals:

- a) $xy + xy'$
- b) $(x + y)(x + y')$
- c) $xyz + x'y + xyz'$
- d) $(A+B)'(A'+B')'$

Solution

$$a) xy + xy' = x(y + y') = x.1 = x$$

$$b) (x+y)(x+y') = xx + xy' + yx + yy' = x + xy' + xy + 0 = x(1 + y' + y) = x.1 = x$$

$$\text{Also } (x+y)(x+y') = x + yy' = x + 0 = x$$

$$c) xyz + x'y + xyz' = xy(z + z') + x'y = xy + x'y = y(x + x') = y$$

$$d) (A+B)'(A'+B')' = (A'B').(AB) = 0$$

Practice! Practice! Practice!

Find the complement of the following expressions:

- a) $xy' + x'y$
- b) $(AB' + C)D' + E$
- c) $(x + y' + z)(x' + z')(x + y)$

Solution

$$\text{a) } [xy' + x'y]' = (xy')' \cdot (x'y)' = (x' + y) \cdot (x + y') = \\ xx' + yy' + xy + x'y' = xy + x'y'$$

$$\text{b) } [(AB' + C)D' + E]' = [(AB' + C)D']' \cdot E' = \\ [(AB' + C)' + D] \cdot E' = [(A' + B) \cdot C' + D] \cdot E'$$

$$\text{c) } [(x + y' + z)(x' + z')(x + y)]' = \\ (x + y' + z)' + (x' + z')' + (x + y)' = x'yz' + xz + x'y'$$

Practice time

- Solve : 2-5, 2-6, 2-11
(Morris Mano chapter 2)