

---

# Sequential Circuit Design

---

# Sequential Logic Design

---

## Contents

- Why sequential logic?
- Flip-flop criteria table
- Sequential circuit analysis
- Sequential circuit design

# Why Sequential Logic?

- Sequential circuit has **additional dimension** which is **time**
- Combinational logic only depends on current input
- Sequential circuit output depends on previous input other than current input
- **More powerful** than combination logic
- Able to model condition which can't be modeled by combinational logic

# Sequential Circuit Analysis

- Given sequential circuit diagram, behavioral analysis from **state table** and also **state diagram**
- Need state equations to get **flip-flop input** and **output functions** for circuit output other than flip-flop (if any)
- We use  $A(t)$  and  $A(t+1)$  to represent current condition and the next condition for flip-flop represented by  $A$ .
- Other method, we can use  $A$  and  $A^+$  to represent current condition and the following condition

# Types of tables in sequential circuit

- Characteristic table
- Criteria Table
- State Table
- Excitation table

$Q(t)$	$S$	$R$	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	indeterminate
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	indeterminate

$J$	$K$	$Q(t+1)$	Comments
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q(t)'$	Toggle

Present state		Input $x$	Next state		Flip-flop inputs			
$A$	$B$		$A^+$	$B^+$	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1


Present State		Input $x$	Next State		Output $y$
$A$	$B$		$A^+$	$B^+$	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

# Flip-flop Excitation Tables: Terminology (1)

- **Analysis:** Start from circuit diagram, **build state table** or state diagram
- **Design:** Start from specification set (i.e. in state equation form, state table or state diagram) **build logic circuit.**
- Criteria table is used in analysis
- Excitation tables is used in design

# Sequential Circuit Analysis: Equations
 
### Example 1: Find the input equation for flip-flops (using D flip-flop) and output equation



# Sequential Circuit Analysis: Equations

## ■ Example 1 (using D flip-flop)

State equation

$$DA = A.x + B.x$$

$$DB = A'.x$$


Output Function

$$y = (A + B).x'$$

Flip-flop input

External input

Present state

 

*Note:*  
 $A+$  or  $A(t+1)$ : both  
refer to next state of  
flipflop



# Sequential Circuit Analysis: State Table

- From the state equations and output function, we can derive state table which contains all combined binary available for current condition and input
- **State table**
  - The same as Truth Table
  - Input and condition pad on the left
  - Output and next condition on the right
  - combined binary available for current condition and input
- **M flip-flop and n input  $\Rightarrow 2^{m+n}$  line**

# Sequential Circuit Analysis

State equation

$$A^+ = A.x + B.x$$

$$B^+ = A'.x$$

Output function

$$y = (A + B).x'$$

State table for circuit in Example 1

Present State		Input $x$	Next State		Output $y$	FF Inputs	
$A$	$B$		$A^+$	$B^+$		DA	DB
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1
0	1	0	0	0	1	0	0
0	1	1	1	1	0	1	1
1	0	0	0	0	1	0	0
1	0	1	1	0	0	1	0
1	1	0	0	0	1	0	0
1	1	1	1	0	0	1	0

# Sequential Circuit Analysis

Present State		Input	Next State		Output
A	B		A <sup>+</sup>	B <sup>+</sup>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Other method

Present State	Next State		Output	
	x=0	x=1	x=0	x=1
AB	A <sup>+</sup> B <sup>+</sup>	A <sup>+</sup> B <sup>+</sup>	y	y
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0


# Sequential Circuit Analysis

- From the truth table, we can draw state diagram
- State diagram
  - Each state is represented by circle
  - Each arrow (between two circle) represent transfer for sequential logic (i.e. line transition in truth table)
  - a/b label for each arrow where a represent inputs and b represent output for circuit in transition
- Each flip-flop value combination represent state. Therefore, **m flip-flop=> until  $2^m$  state.**

# Sequential Circuit Analysis: State Diagram

Present State	Next State		Output	
	$x=0$	$x=1$	$x=0$	$x=1$
$AB$	$A^+B^+$	$A^+B^+$	$y$	$y$
00	00	01	0	0
01	00	11	1	0
10	00	10	1	0
11	00	10	1	0

State diagram for circuit in example 1

 

# Flip-flop Input Function


- Output of sequential circuit is function for current condition for flip-flop and input. This is explained using algebra by circuit output function
  - In example 1:  $y = (A+B)x'$
- Circuit part that generate input to flip-flop is explained using algebra by flip-flop input functions

# Flip-flop Input Function

- Flip-flop input function determine next condition
- From flip-flop input function and criteria table for flip-flop, we get next condition of the flip-flop

# Flip-flop Input Function

 - Example 2: Find flip-flop input equation in circuit with JK flip flop






# Flip-flop Input Function


- Example 2: Find flip-flop input equation in circuit with JK flip flop
- We **use 2 character** to represent **flip-flop input**: first character represent flip-flop input (J or K for JK flip-flop, S or R for SR flip-flop, D for D flip-flop, T for T flip-flop ) and second character represent name of the flip-flop

$$JA = B.C'.x + B'.C.x'$$
$$KA = B + y$$

 

 
# Analysis: Example 3

- Given sequential circuit with two JK flip-flop, A and B and one input x


 
# Analysis: Example 3

- Given sequential circuit with two JK flip-flop, A and B and one input x



- Get the input flip-flop function from the circuit

$$\begin{aligned} JA &= B \\ KA &= B.x' \end{aligned}$$

$$\begin{aligned} JB &= x' \\ KB &= A'.x + A.x' = A \oplus x \end{aligned}$$

# Analysis: Example 3

- Input flip-flop function

$$JA = B$$

$$KA = B.x'$$

$$JB = x'$$

$$KB = A'.x + A.x' = A \oplus x$$

- Fill the state table with the above function using criteria table for used flip-flop


J	K	$Q(t+1)$	Comments
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q(t)'$	Toggle

Present state		Input $x$	Next state		Flip-flop inputs			
$A$	$B$		$A^+$	$B^+$	$JA$	$KA$	$JB$	$KB$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

# Analysis: Example 3

- Draw state diagram from the state table

Present state		Input $x$	Next state		Flip-flop inputs			
$A$	$B$		$A^+$	$B^+$	$JA$	$KA$	$JB$	$KB$
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

 

# Flip-flop Excitation Tables: Terminology (2)

- **Analysis:** Start from circuit diagram, **build state table** or state diagram
- **Design:** Start from specification set (i.e. in state equation form, state table or state diagram) **build logic circuit.**
- Criteria table is used in analysis
- Excitation tables is used in design

# Flip-flop Excitation Tables

- Excitation tables : it give transition characteristic between current condition and next condition to determine flip-flop input

$Q$	$Q^+$	$J$	$K$
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

JK Flip-flop

$Q$	$Q^+$	$S$	$R$
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

SR Flip-flop

$Q$	$Q^+$	$D$
0	0	0
0	1	1
1	0	0
1	1	1

D Flip-flop


$Q$	$Q^+$	$T$
0	0	0
0	1	1
1	0	1
1	1	0

T Flip-flop

# How to build excitation table:

## Example: JK Flip-Flop

Q	Q+	Actually what happens		Final Combined Result	
		J	K	J	K
0	0	0	1	0	x
		0	0		
0	1	1	0	1	x
		1	1		
1	0	0	1	x	1
		1	1		
1	1	0	0	x	0
		1	0		

 

Q	Q*	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

JK Flip-flop




# Designing Sequential Circuit

## Design steps

- Step 1: Start with circuit specification – characteristic of circuit
- Step 2: Build state table
- (Ignore) Do state reduction if needed (not in syllabus)
- (Ignore) Do state assignment (not in syllabus)
- Step 3: Determine number of flip-flop which will be used
- Step 4: Build circuit excitation and output table from state table
- Step 5: Build circuit output function and flip-flop input function
- Step 6: Draw logic diagram

 
# Design: Example 1

- Given state diagram as follows, get the sequential circuit using JK flip-flop


 
# Design: Example 1

- State/excitation table using JK flip-flop



Present State <i>AB</i>	Next State	
	<i>x=0</i>	<i>x=1</i>
00	00	01
01	10	01
10	10	11
11	11	00

<i>Q</i>	<i>Q*</i>	<i>J</i>	<i>K</i>
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

JK Flip-flop's excitation table.

Present state		Input <i>x</i>	Next state		Flip-flop inputs			
<i>A</i>	<i>B</i>		<i>A*</i>	<i>B*</i>	<i>JA</i>	<i>KA</i>	<i>JB</i>	<i>KB</i>
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

Note:

**Step 1:** Build state table

**Step 2:** Find no. of Flip-Flop (*i.e.*  $2^m$  states means *m* flip-flops)


**Step 3:** Build Excitation table

**Step 4:** Use K-map to find input functions

**Step 5:** Design logic diagram

# Design: Example 1





- Block diagram

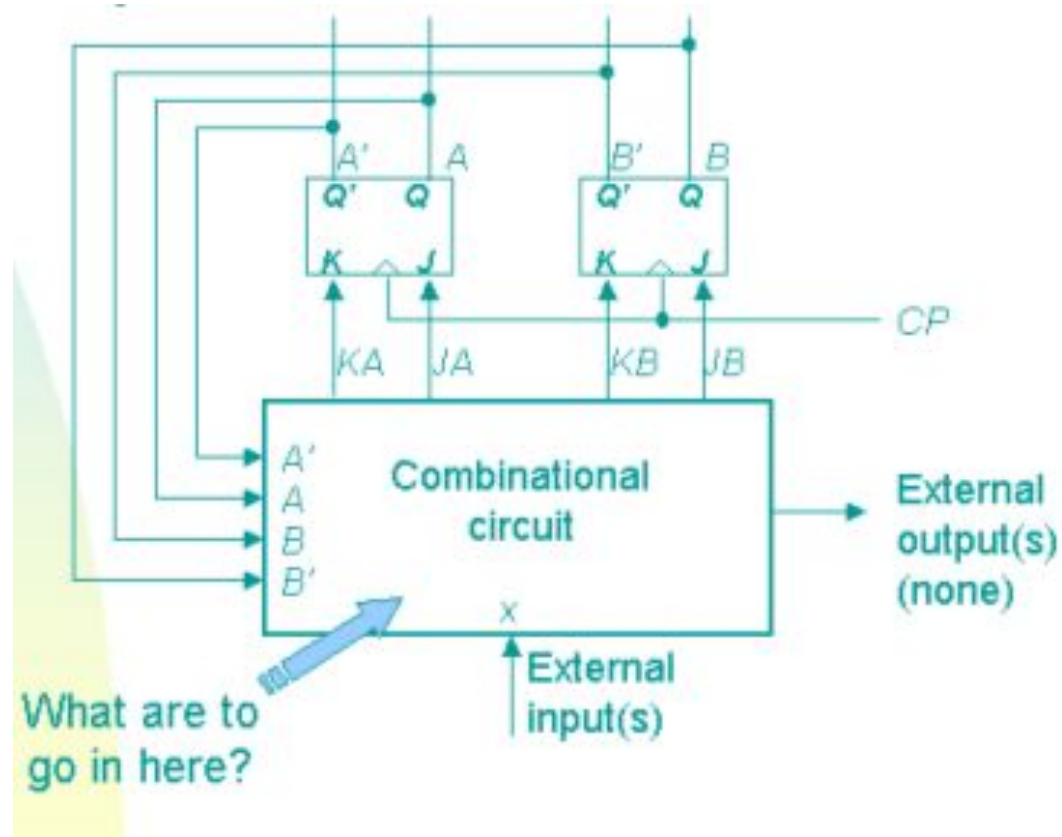

# Design: Example 1

- From state table, get input flip-flop function

Present state		Input $x$	Next state		Flip-flop inputs			
$A$	$B$		$A^+$	$B^+$	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

    


# Design: Example 1

- Input flip-flop function

$$JA = B.x'$$
$$KA = B.x$$

$$JB = x$$
$$KB = (A \oplus x)'$$

- Logic Diagram

 

# Design: Example 2

- Design, using D flip-flop, circuit is based on state table below. (Exercise: How if using JK flip-flop)

Present state		Input	Next state		Output
A	B		A <sup>+</sup>	B <sup>+</sup>	
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

# Design: Example 2

- Determine input expression for flip-flop and y output


Note: D-FF is too trivial for including it in the excitation table

Present state		Input $x$	Next state		Output $y$
$A$	$B$		$A^+$	$B^+$	
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

$$DA(A, B, x) = \sum m(2,4,5,6)$$

$$DB(A, B, x) = \sum m(1,3,5,6)$$


$$y(A, B, x) = \sum m(1,5)$$

 



 
# Design: Example 2

- From expression built, draw logic diagram



 
# Introduction: Counters

- **Counters** are circuits that cycle through a specified number of states.
- Two types of counters:
  - ❖ synchronous (parallel) counters
  - ❖ asynchronous (ripple) counters
- Ripple counters allow some flip-flop outputs to be used as a source of clock for other flip-flops.
- Synchronous counters apply the same clock to all flip-flops.


 
# Synchronous (Parallel) Counters

- **Synchronous (parallel) counters:** the flip-flops are clocked at the same time by a common clock pulse.
- We can design these counters using the sequential logic design process.
- Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).



Present state		Next state		Flip-flop inputs	
$A_1$	$A_0$	$A_1^+$	$A_0^+$	$TA_1$	$TA_0$
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1


# Synchronous (Parallel) Counters

- Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).

Present state		Next state		Flip-flop inputs	
$A_1$	$A_0$	$A_1^+$	$A_0^+$	$TA_1$	$TA_0$
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

$$TA_1 = A_0$$


$$TA_0 = 1$$

 


# Synchronous (Parallel) Counters

- Example: 3-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J, K inputs).


Present state			Next state			Flip-flop inputs		
$A_2$	$A_1$	$A_0$	$A_2^+$	$A_1^+$	$A_0^+$	$TA_2$	$TA_1$	$TA_0$
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

 

$$TA_2 = A_1 \cdot A_0$$

 

$$TA_1 = A_0$$

 

$$TA_0 = 1$$



# Synchronous (Parallel) Counters

- Example: 3-bit synchronous binary counter (cont'd).

$$TA_2 = A_1 \cdot A_0$$

$$TA_1 = A_0$$

$$TA_0 = 1$$

  

# Synchronous (Parallel) Counters

- Note that in a binary counter, the  $n^{\text{th}}$  bit (shown underlined) is always complemented whenever

$$\underline{0}11\dots11 \rightarrow \underline{1}00\dots00$$


$$\text{or } \underline{1}11\dots11 \rightarrow \underline{0}00\dots00$$

- Hence,  $X_n$  is complemented whenever

$$X_{n-1}X_{n-2}\dots X_1X_0 = 11\dots11.$$

- As a result, if T flip-flops are used, then
 
$$TX_n = X_{n-1} \cdot X_{n-2} \cdot \dots \cdot X_1 \cdot X_0$$



# Synchronous (Parallel) Counters


- Example: 4-bit synchronous binary counter.

$$TA_3 = A_2 \cdot A_1 \cdot A_0$$

$$TA_2 = A_1 \cdot A_0$$

$$TA_1 = A_0$$

$$TA_0 = 1$$

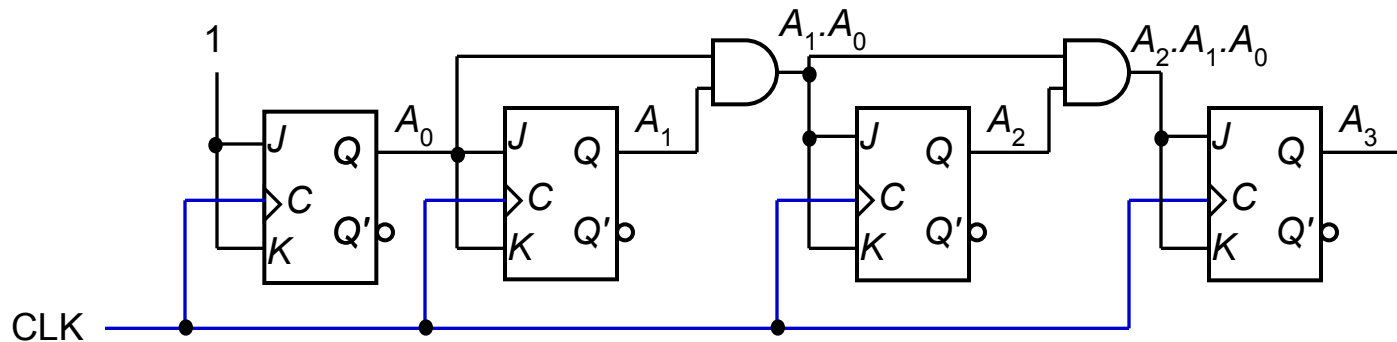



# Synchronous (Parallel) Counters

## SELF STUDY

- Example: Synchronous decade/BCD counter.

Clock pulse	$Q_3$	$Q_2$	$Q_1$	$Q_0$
Initially	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10 (recycle)	0	0	0	0

$$T_0 = 1$$

$$T_1 = Q_3' \cdot Q_0$$

$$T_2 = Q_1 \cdot Q_0$$

$$T_3 = Q_2 \cdot Q_1 \cdot Q_0 + Q_3 \cdot Q_0$$

[https://www.youtube.com/watch?v=fKVZpupyP\\_o&list=PLBlnK6fEyqRjMH3mWf6kwqiTbT798eAOm&index=186](https://www.youtube.com/watch?v=fKVZpupyP_o&list=PLBlnK6fEyqRjMH3mWf6kwqiTbT798eAOm&index=186)

# Synchronous (Parallel) Counters


- Example: Synchronous decade/BCD counter (cont'd).

$$T_0 = 1$$

$$T_1 = Q_3' \cdot Q_0$$


$$T_2 = Q_1 \cdot Q_0$$
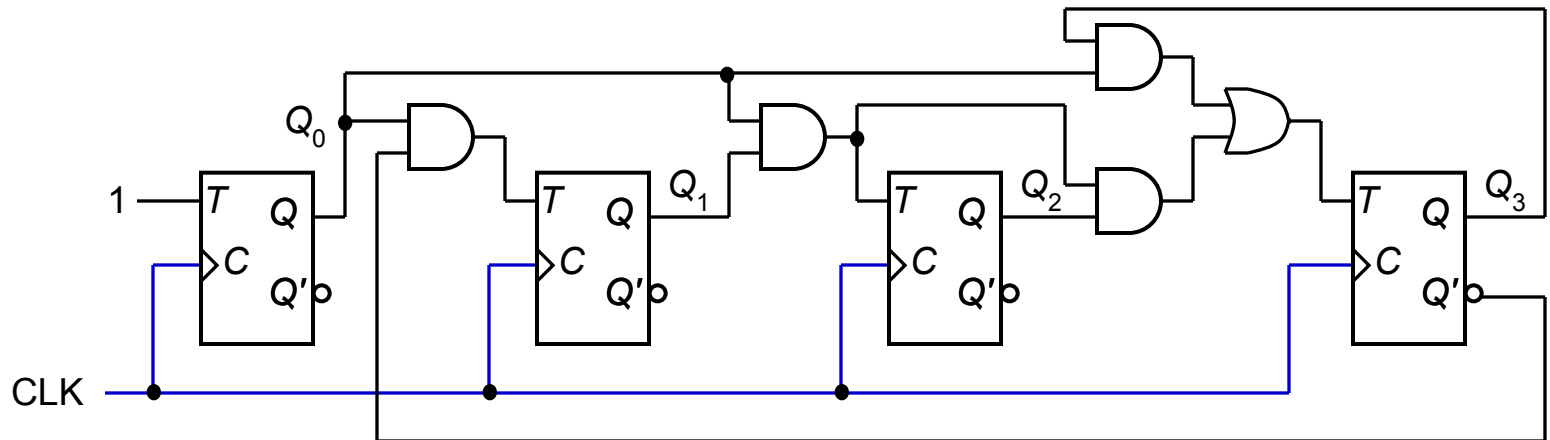
$$T_3 = Q_2 \cdot Q_1 \cdot Q_0 + Q_3 \cdot Q_0$$


 
# Up/Down Synchronous Counters

- **Up/down synchronous counter:** a *bidirectional* counter that is capable of counting either up or down.
- An input (control) line *Up/Down* (or simply *Up*) specifies the direction of counting.
  - ❖  $Up/Down = 1 \rightarrow$  Count upward
  - ❖  $Up/Down = 0 \rightarrow$  Count downward



# 5-BIT Up/Down Synchronous Counter

Control 1/p M	P.S. Q <sub>C</sub> <sup>+</sup> Q <sub>B</sub> <sup>+</sup> Q <sub>A</sub> <sup>+</sup>			M.C. Q <sub>C</sub> <sup>+</sup> Q <sub>B</sub> <sup>+</sup> Q <sub>A</sub> <sup>+</sup>			1/p of FF T <sub>C</sub> T <sub>B</sub> T <sub>A</sub>			M=0 up M=1 down
	Q <sub>C</sub> <sup>+</sup>	Q <sub>B</sub> <sup>+</sup>	Q <sub>A</sub> <sup>+</sup>	Q <sub>C</sub> <sup>+</sup>	Q <sub>B</sub> <sup>+</sup>	Q <sub>A</sub> <sup>+</sup>	T <sub>C</sub>	T <sub>B</sub>	T <sub>A</sub>	
0	0	0	0	0	0	1	0	0	1	up counting
0	0	0	1	0	1	0	0	1	1	
0	0	1	0	0	1	1	0	0	1	
0	0	1	1	1	0	0	1	1		
0	1	0	0	1	0	1	0	0		
0	1	0	1	1	1	0	0	1		
0	1	1	0	1	1	1	0	0		
0	1	1	1	0	0	0	1	1		
1	0	0	0							
1	0	0	1							

<https://www.youtube.com/watch?v=svFUEJkoeVY&list=PLBlnK6fEyqRjMH3mWf6kwqiTbT798eAOm&index=189>

# Up/Down Synchronous Counters

- Example: A 3-bit up/down synchronous binary counter.

Clock pulse	<i>Up</i>	$Q_2$	$Q_1$	$Q_0$	<i>Down</i>
0		0	0	0	
1		0	0	1	
2		0	1	0	
3		0	1	1	
4		1	0	0	
5		1	0	1	
6		1	1	0	
7		1	1	1	

$$TQ_0 = 1$$

$$TQ_1 = (Q_0 \cdot Up) + (Q_0' \cdot Up')$$

$$TQ_2 = (Q_0 \cdot Q_1 \cdot Up) + (Q_0' \cdot Q_1' \cdot Up')$$

Up counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0$$

$$TQ_2 = Q_0 \cdot Q_1$$

Down counter

$$TQ_0 = 1$$

$$TQ_1 = Q_0'$$

$$TQ_2 = Q_0' \cdot Q_1'$$


# Up/Down Synchronous Counters

- Example: A 3-bit up/down synchronous binary counter (cont'd).

$$TQ_0 = 1$$



$$TQ_1 = (Q_0 \cdot Up) + (Q_0' \cdot Up')$$
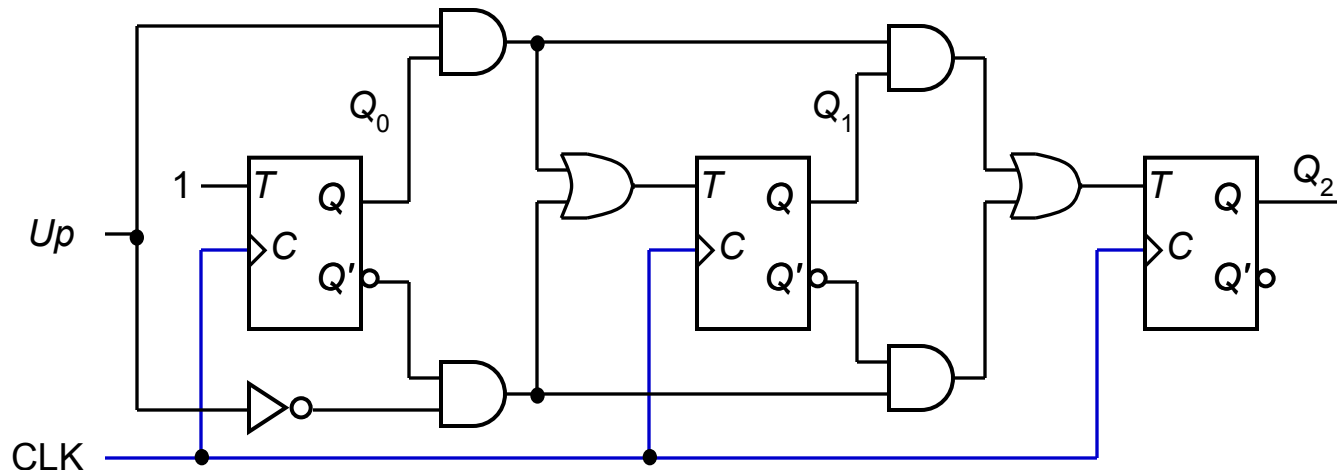
$$TQ_2 = (Q_0 \cdot Q_1 \cdot Up) + (Q_0' \cdot Q_1' \cdot Up')$$



  
# PRACTICE PROBLEM

- Implement the following counter using T FF  
1->2->3->5->7->11->13->1




# PRACTICE PROBLEM

	$A_3$	$A_2$	$A_1$	$A_0$	$A_3^+$	$A_2^+$	$A_1^+$	$A_0^+$	$TA_3$	$TA_2$	$TA_1$	$TA_0$
0	0	0	0	0	0	0	0	1	0	0	0	1
1	0	0	0	1	0	0	1	0	0	0	1	1
2	0	0	1	0	0	0	1	1	0	0	0	1
3	0	0	1	1	0	1	0	1	0	1	1	0
4	0	1	0	0	0	0	0	1	0	1	0	1
5	0	1	0	1	0	1	1	1	0	0	1	0
6	0	1	1	0	0	0	0	1	0	1	1	1
7	0	1	1	1	1	0	1	1	1	1	0	0
8	1	0	0	0	0	0	0	1	1	0	0	1
9	1	0	0	1	0	0	0	1	1	0	0	0
10	1	0	1	0	0	0	0	1	1	0	1	1
11	1	0	1	1	1	1	0	1	0	1	1	0
12	1	1	0	0	0	0	0	1	1	1	0	1
13	1	1	0	1	0	0	0	1	1	1	0	0
14	1	1	1	0	0	0	0	1	1	1	1	1
15	1	1	1	1	0	0	0	1	1	1	1	0

 



# PRACTICE PROBLEM

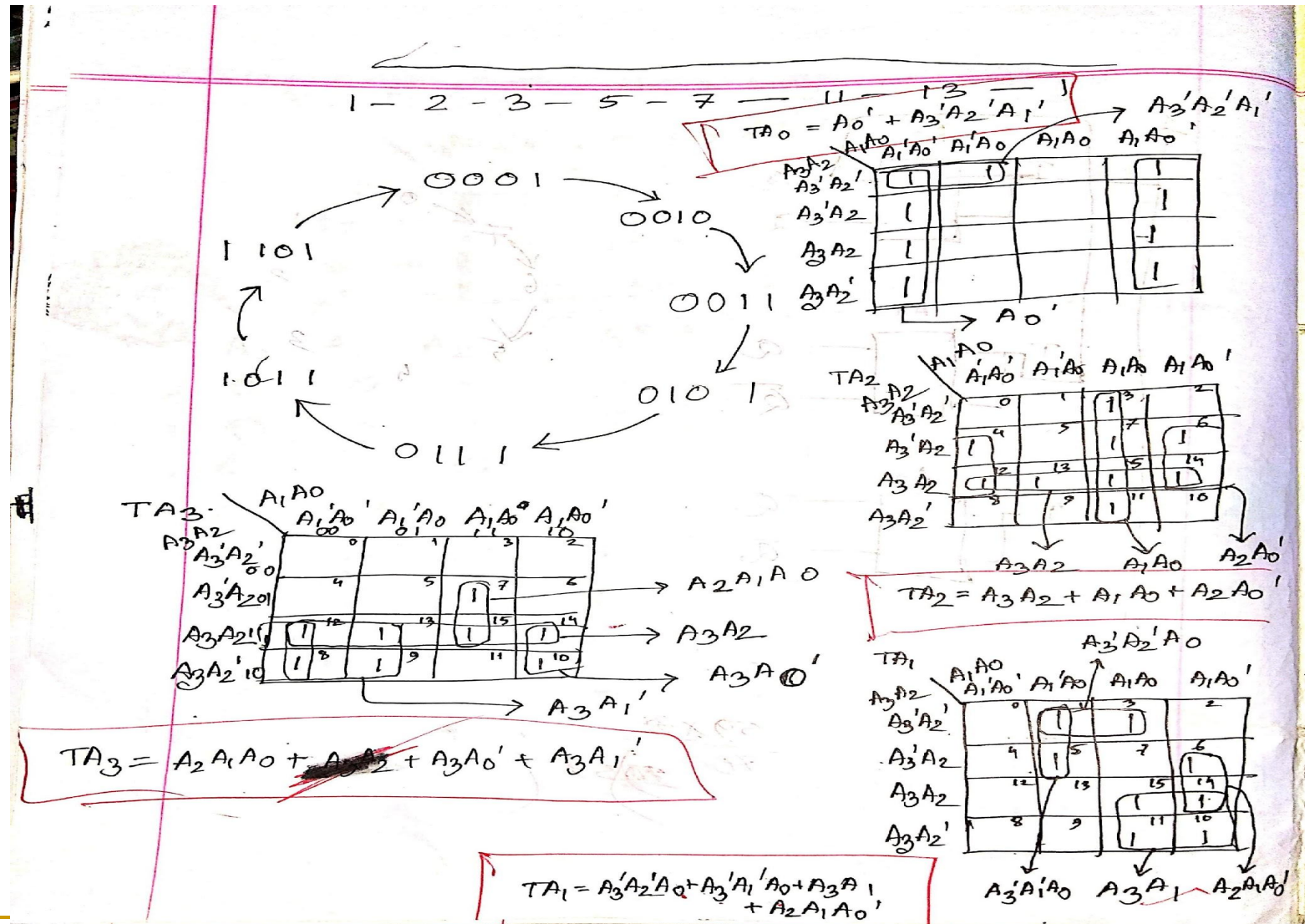

# PRACTICE PROBLEM

- Implement the following counter using D FF  
Green->Yellow->Red->Yellow->Green

Assuming  
Green  $\rightarrow 00$   
Yellow  $\rightarrow 01$   
Red  $\rightarrow 10$

A	B	$z$	$A^+$	$B^+$	$DA$	$DB$
0	0	0	0	1	0	1
0	0	1	0	1	0	1
0	1	0	0	0	0	0
0	1	1	1	0	1	0
1	0	0	0	1	0	1
1	0	1	0	1	0	1
1	1	0	X	X	X	X
1	1	1	X	X	X	X

$DA = Bz$

$DB = \overline{B}$

# Asynchronous (Ripple) Counters



- **Asynchronous counters**: the flip-flops do not change states at exactly the same time as they do not have a common clock pulse.
- Also known as **ripple counters**, as the input clock pulse “ripples” through the counter – cumulative delay is a drawback.



This counter is also a *frequency divider*.

# Asynchronous (Ripple) Counters

  - Example: 2-bit ripple binary counter.
- Output of one flip-flop is connected to the clock input of the next more-significant flip-flop.





Timing diagram

00 → 01 → 10 → 11 → 00 ...

# Asynchronous (Ripple) Counters

- Example: 3-bit ripple binary counter.

  

# Asynchronous (Ripple) Counters

- Example: 4-bit ripple binary counter (negative-edge triggered).

