

CSE 260

Digital Logic Design


Combinational Circuit-3

BRAC University

Arithmetic Circuits: Comparator

- **Magnitude comparator**: compares 2 values A and B, to see if $A > B$, $A = B$ or $A < B$.
- How do we compare two 4-bit values A ($a_3a_2a_1a_0$) and B ($b_3b_2b_1b_0$)?
 - If ($a_3 > b_3$) then $A > B$
 - If ($a_3 < b_3$) then $A < B$
 - If ($a_3 = b_3$) then if ($a_2 > b_2$)


Equality Comparator

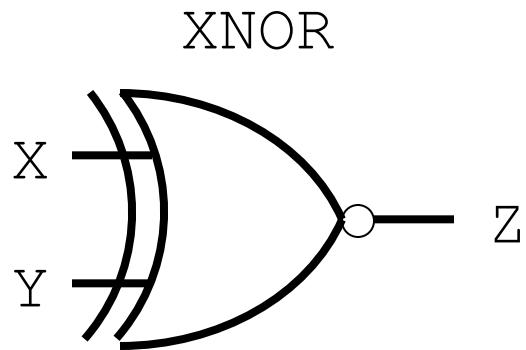

$$Z = \neg (X \oplus Y)$$

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

4-Bit Equality Comparator

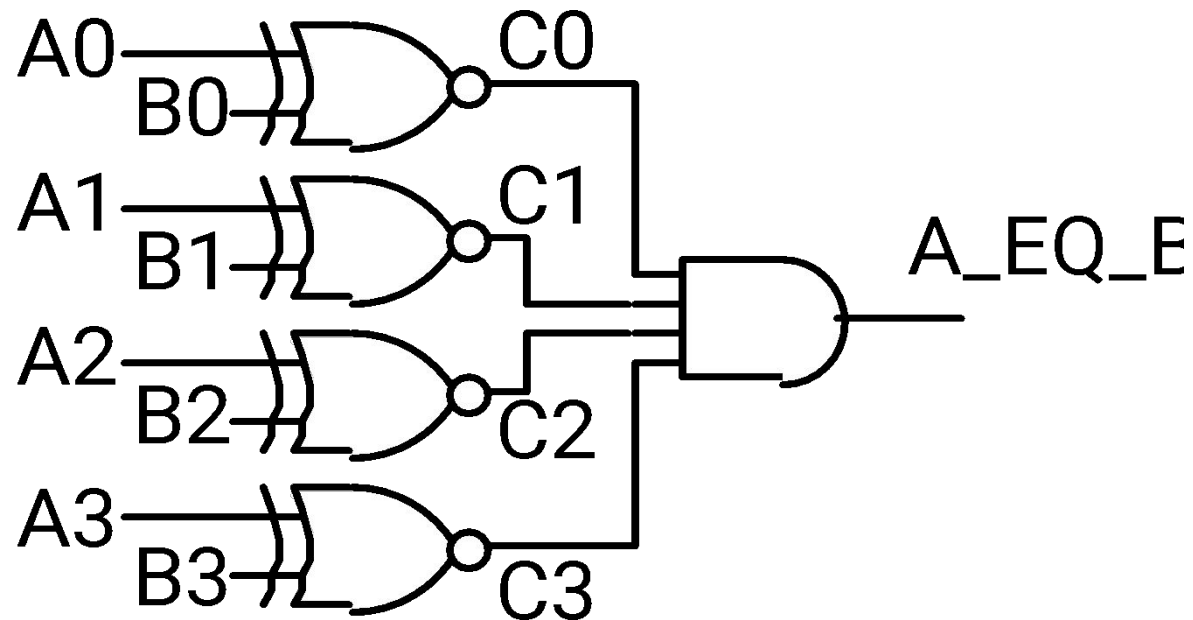


FIELD A = [A0..3];


FIELD B = [B0..3];

FIELD C = [C0..3];

4-bit Equality Detector

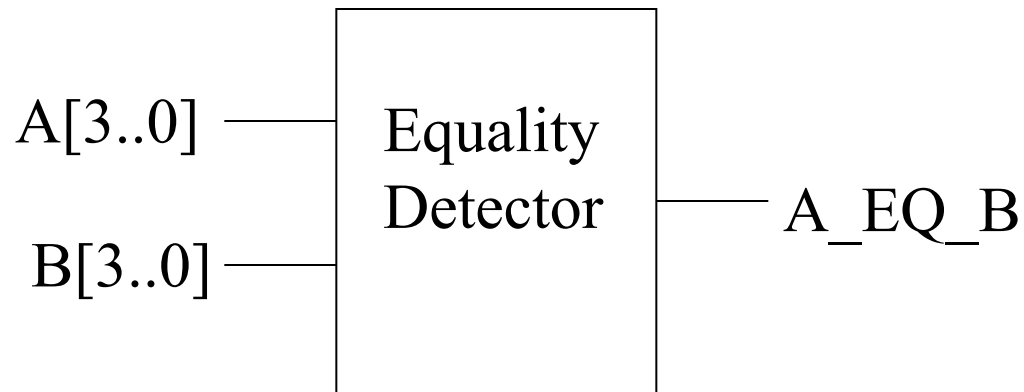


4-bit Magnitude Comparator

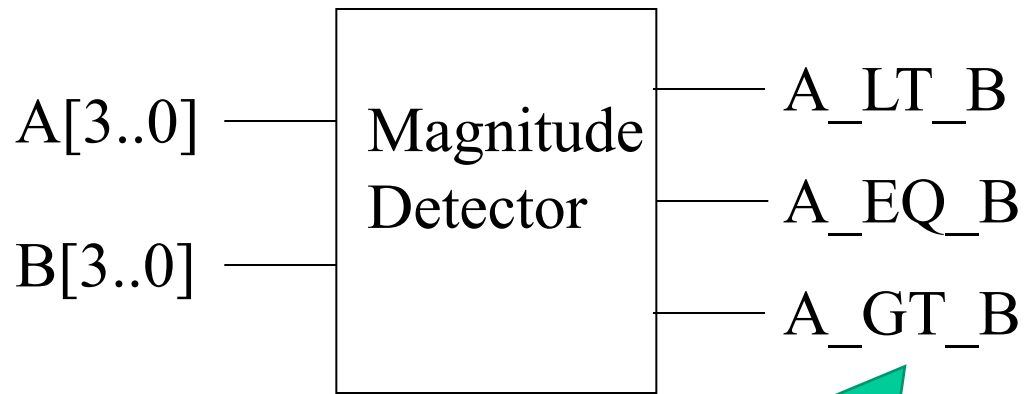

Note: here EQ stands for 'equal',
LT stands for 'less than' and GT
stands for 'greater than'.

Magnitude Comparator

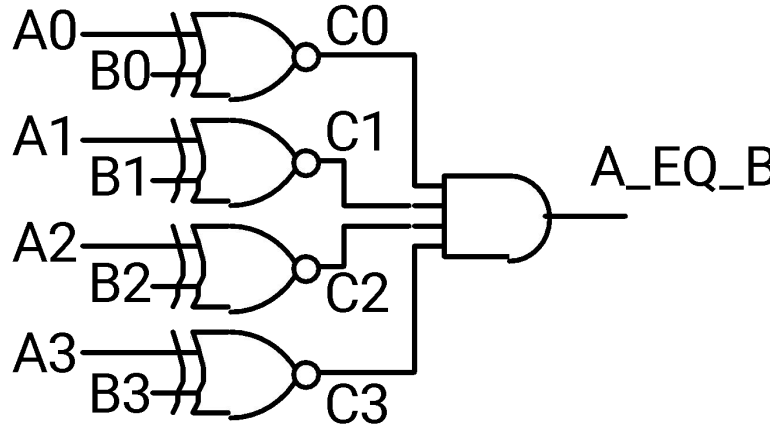


How can we find A_GT_B?

How many rows would a truth table have?

$$2^8 = 256!$$

Magnitude Comparator

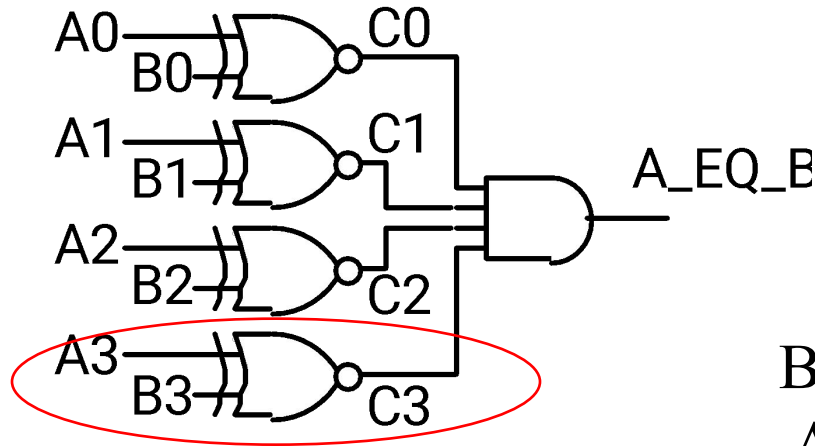


Find A_GT_B

**If A = 1001 and
B = 0111
is A > B?
Why?**

Because $A_3 > B_3$, which means
 $A=1$ and $B=0$
i.e. $A_3 \& !B_3 = 1$

Therefore, one term in the
logic equation for A_GT_B is
 $A_3 \& !B_3$

Magnitude Comparator

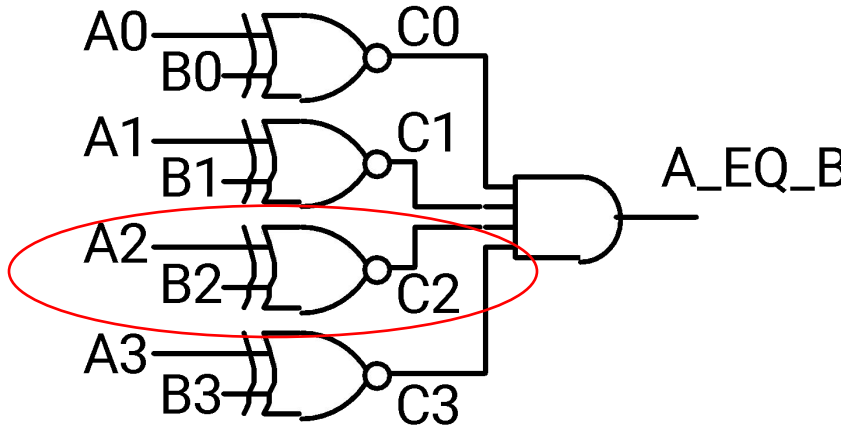

**If A = 1101 and
B = 1011
is A > B?
Why?**


$$A_GT_B = A3 \& !B3 \\ + \dots$$

Because $A3 = B3$ and
 $A2 > B2$

i.e. $C3 = 1$ and
 $A2 \& !B2 = 1$

Therefore, the next term in the
logic equation for A_GT_B is
 $C3 \& A2 \& !B2$

Magnitude Comparator

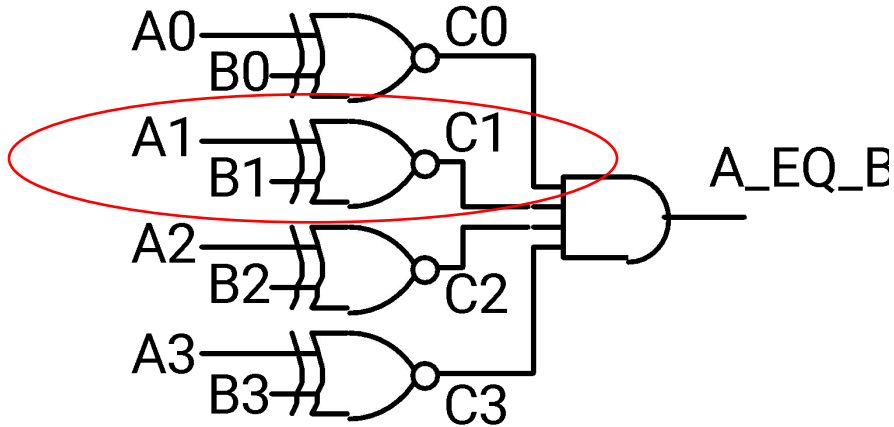

**If A = 1010 and
B = 1001
is A > B?
Why?**


$$A_GT_B = A3 \& !B3 \\ + C3 \& A2 \& !B2 \\ + \dots$$

Because $A3 = B3$ and
 $A2 = B2$ and
 $A1 > B1$

i.e. $C3 = 1$ and $C2 = 1$ and
 $A1 \& !B1 = 1$

Therefore, the next term in the
logic equation for A_GT_B is
 $C3 \& C2 \& A1 \& !B1$

Magnitude Comparator

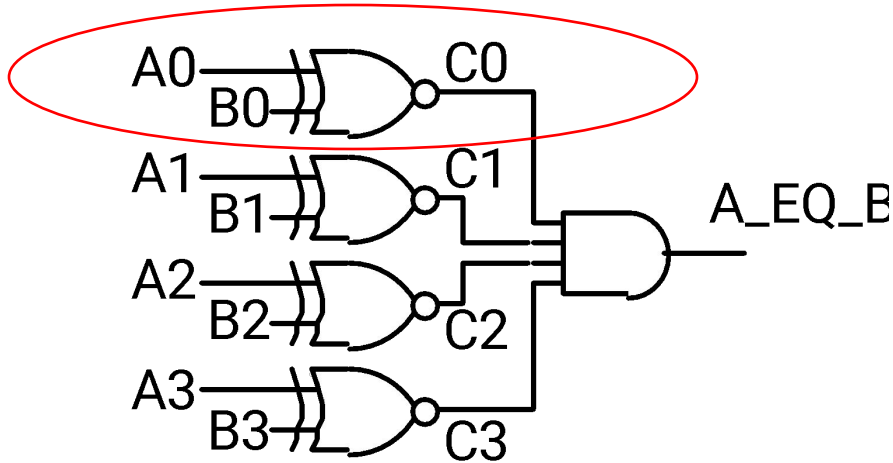

**If A = 1011 and
B = 1010
is A > B?
Why?**


$$\begin{aligned} A_GT_B = & A3 \& !B3 \\ & + C3 \& A2 \& !B2 \\ & + C3 \& C2 \& A1 \& !B1 \\ & + \dots \end{aligned}$$

Because $A3 = B3$ and
 $A2 = B2$ and
 $A1 = B1$ and
 $A0 > B0$

i.e. $C3 = 1$ and $C2 = 1$ and
 $C1 = 1$ and $A0 \& !B0 = 1$


Therefore, the last term in the
logic equation for A_GT_B is
 $C3 \& C2 \& C1 \& A0 \& !B0$

Magnitude Comparator

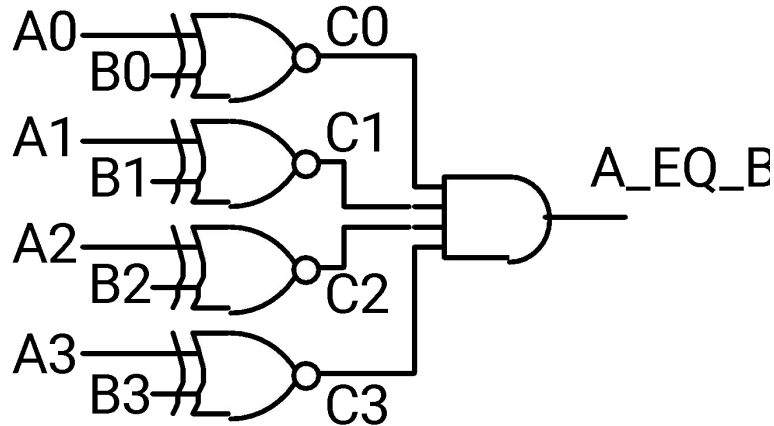

$$\begin{aligned} \mathbf{A_GT_B} = & \mathbf{A3 \& !B3} \\ & \mathbf{+ C3 \& A2 \& !B2} \\ & \mathbf{+ C3 \& C2 \& A1 \& !B1} \\ & \mathbf{+ C3 \& C2 \& C1 \& A0 \& !B0} \end{aligned}$$

Magnitude Comparator

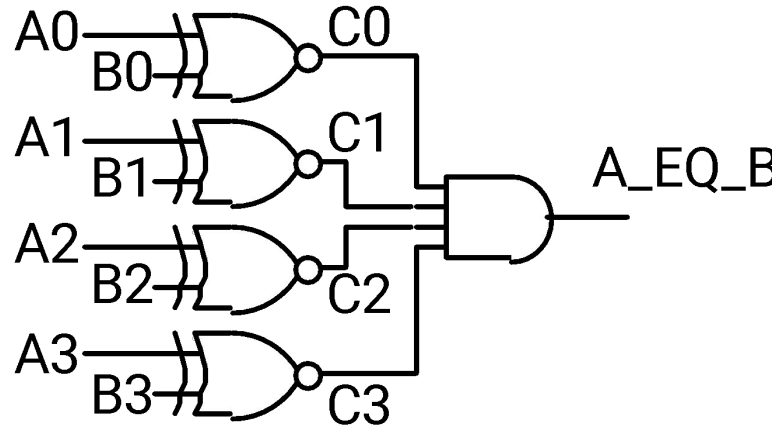


**Now Find
A_LT_B**

$$\begin{aligned} A_LT_B = & !A3 \& B3 \\ & + C3 \& !A2 \& B2 \\ & + C3 \& C2 \& !A1 \& B1 \\ & + C3 \& C2 \& C1 \& !A0 \& B0 \end{aligned}$$

Arithmetic Circuits: Comparator

Let $A = A_3A_2A_1A_0$, $B = B_3B_2B_1B_0$; $x_i = A_i \cdot B_i + A_i' \cdot B_i'$

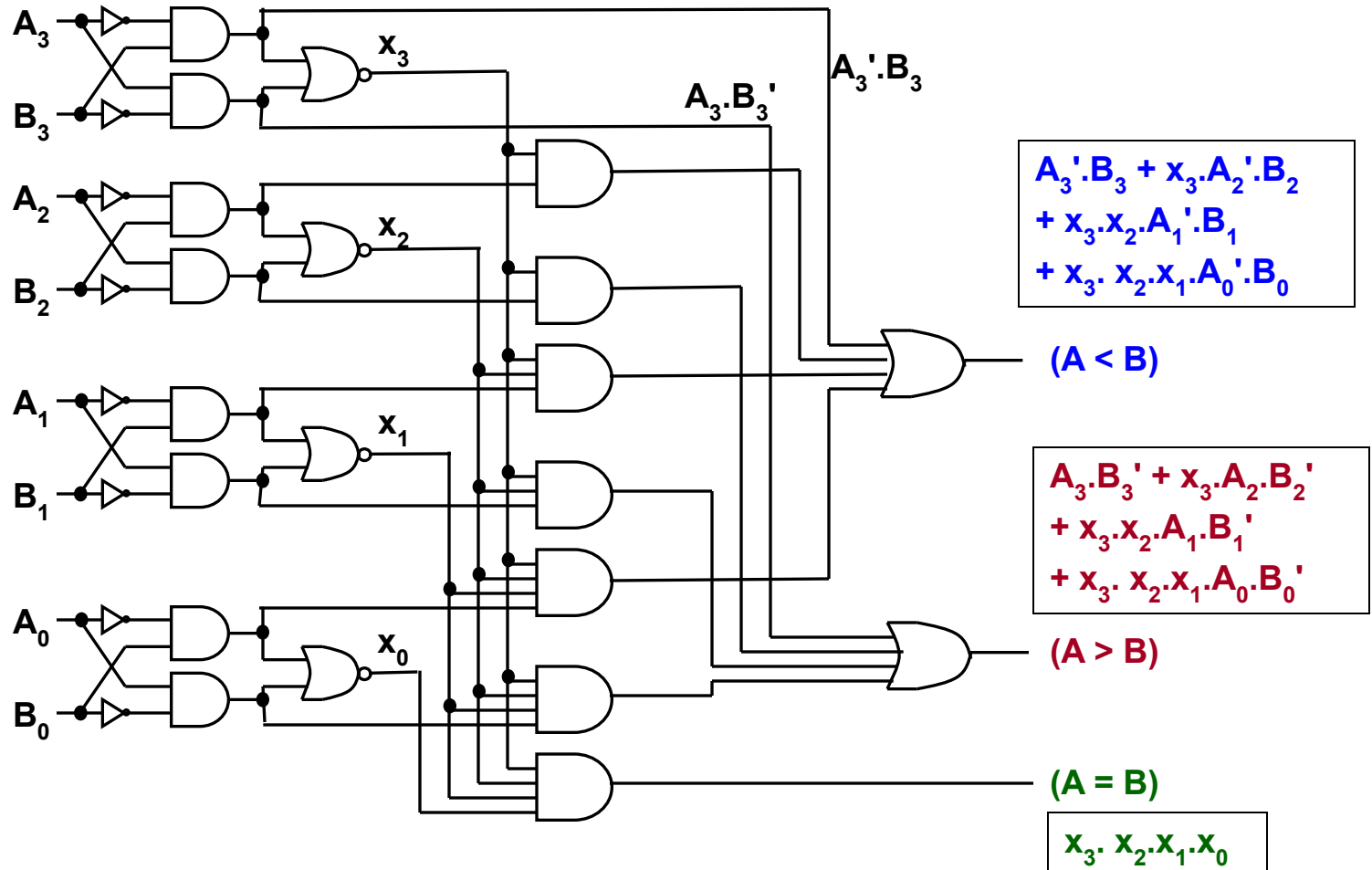
Note: This is the circuit of Magnitude compar-ator !!!
All previous slides where for just understand-ing!



Important points

- **Note: We start by comparing digits in from MSB position. If those digits are equal, then we compare next 2 lower significant pairs of digits.**
- Same circuit of previous slide can be used for comparing relative magnitude of 2 BCD digits.

Arithmetic Circuits: Comparator

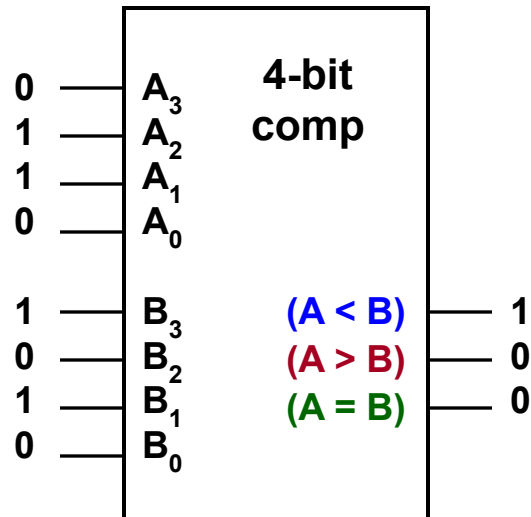

Block diagram of a 4-bit magnitude comparator